

# Diode application : Rectifier

Half-wave  
rectifier


Full-wave  
center tap  
rectifier

Full-wave  
bridge  
rectifier

+ Filters (Capacitor filter)  
only with 'R' load

- ① Ckt diagram
  - ② Working
  - ③ I<sub>p-olp</sub> w.r.t time
  - ④ Analysis :-
- |                                  |                          |
|----------------------------------|--------------------------|
| a) V <sub>out avg</sub>          | { I <sub>out avg</sub> } |
| b) V <sub>out rms</sub>          | { I <sub>out rms</sub> } |
| c) Rectific <sup>n</sup> eff (%) |                          |
| d) Ripple factor (%)             |                          |
| e) TUF                           |                          |

Diode basics:-

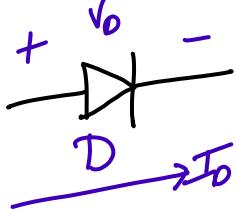

D. is F.B (ON)




D. is R.B (OFF)



## # Half-wave Rectifier with 'R' load:




Circuit diagram:-

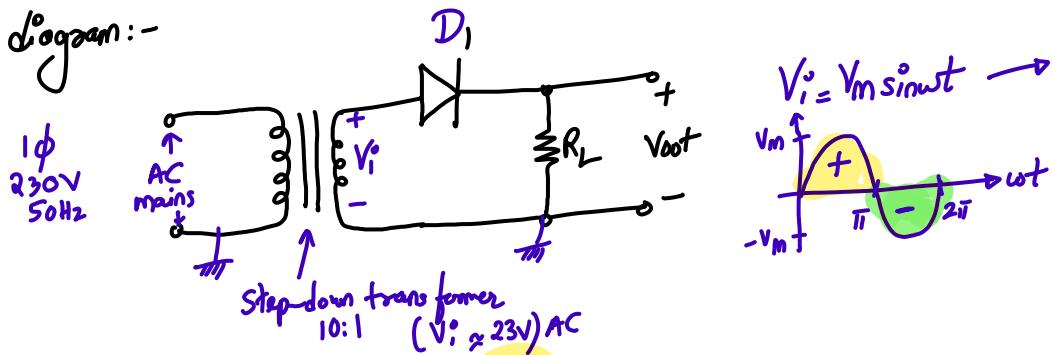

$$V_i = V_m \sin wt \rightarrow \text{Secondary voltage of transformer}$$

Case ①:- During +ve half cycle of  $\frac{1}{2}p(V_i)$


$D_1$  is F.B i.e ON

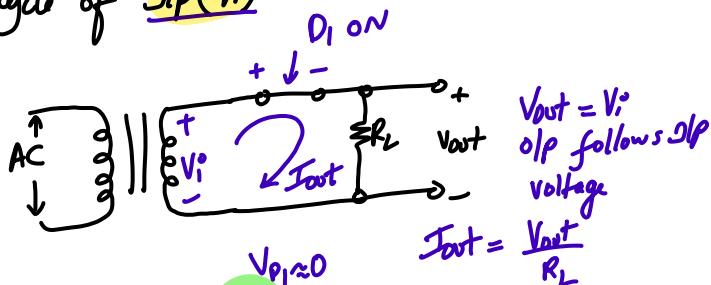

$$V_{out} = V_i \\ \text{o/p follows } \frac{1}{2}p \text{ voltage}$$


Case ②:- During -ve half cycle of  $\frac{1}{2}p(V_i)$

$D_1$  is R.B i.e OFF

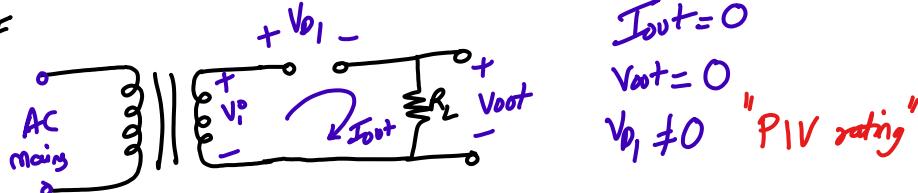

Input-Output wffs :-
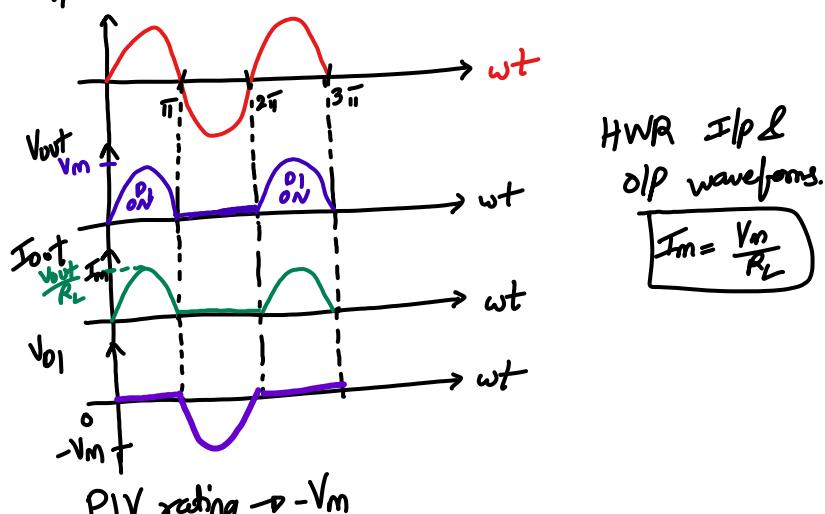
$$\boxed{\begin{aligned} V_{out} &= V_i (\text{if } 0 < wt < \pi) \\ &= 0 \quad \text{if } \pi < wt < 2\pi \end{aligned}} \quad (1)$$



PIV rating  $\rightarrow -V_m$

Analysis (HWR):

- Derive a) Expression for  $V_{out \text{ avg}}$   
 b)  $\pi$  for  $V_{out \text{ rms}}$   
 c)  $\pi$  for rectification efficiency ( $\eta$ )  
 d)  $\pi$  for ripple factor ( $r$ )  
 e)  $\pi$  for TUF

a)  $V_{out(\text{avg})} / V_{dc}$ :

$$V_{out(\text{avg})} = \frac{1}{T} \int_0^T V_{out} dt$$


$$V_{out(\text{avg})} = \frac{1}{2\pi} \int_0^{2\pi} V_{out} dt$$

$$V_{out(\text{avg})} = \frac{1}{2\pi} \left[ \int_0^{\pi} V_m \sin \omega t dt + \int_{\pi}^{2\pi} 0 dt \right]$$

$$V_{out(\text{avg})} = \frac{V_m}{2\pi} \left[ -\cos \omega t \right]_0^{\pi} = -\frac{V_m}{2\pi} [\cos \pi - \cos 0]$$

$$V_{out(\text{avg})} = \frac{V_m}{2\pi} (2)$$
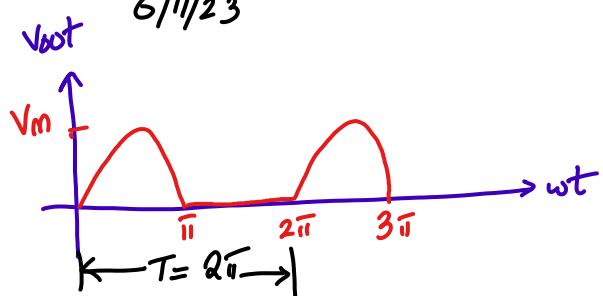
$$V_{out(\text{avg})} = \frac{V_m}{\pi} \quad \text{i.e. } V_{dc} = 0.318 V_m$$




$$V_i = V_m \sin \omega t$$

 $\frac{2\pi}{\pi}$ 

$$\int_0^{\pi} 0 dt$$

$$= -\frac{V_m}{2\pi} [\cos \pi - \cos 0]$$

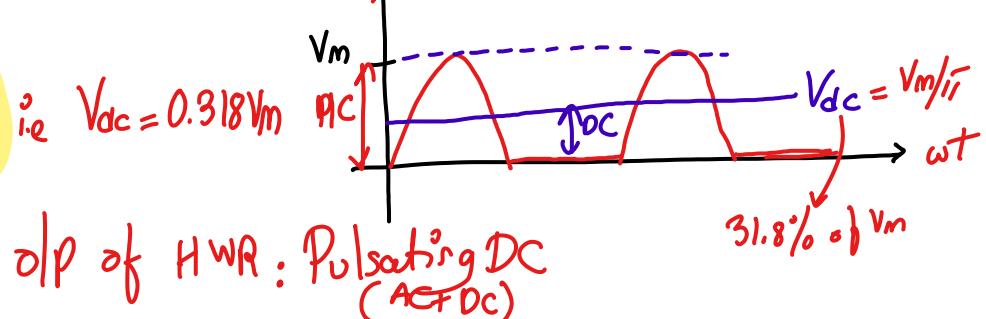 $V_{out}$  $\int_0^{2\pi} V_{out} dt$ 

o/p of HWR: Pulsating DC  
(AC+DC)

$$I_{out(\text{avg})} = I_{dc} = \frac{V_{out(\text{avg})}}{R_L} = \frac{V_{dc}}{R_L} = \frac{V_m}{\pi R_L} I_m$$

$$I_{out(\text{avg})} = \frac{I_m}{\pi} \quad \text{where } I_m = \frac{V_m}{R_L}$$

b)  $V_{out(\text{rms})} \rightarrow$  RMS value of AC component of o/p

$$V_{out}^2(\text{rms}) = \frac{1}{T} \int_0^T V_{out}^2(wt) dt \quad ; \quad T = 2\pi$$

$$V_i = V_m \sin \omega t$$

$$V_{out}^2(\text{rms}) = \frac{1}{2\pi} \int_0^{2\pi} V_{out}^2(wt) dt$$

$$V_{out}^2(\text{rms}) = \frac{1}{2\pi} \int_0^{\pi} V_m^2 \sin^2 \omega t dt = \frac{V_m^2}{2\pi} \int_0^{\pi} \left(1 - \frac{\cos 2\omega t}{2}\right) dt$$

$$V_{out}^2(\text{rms}) = \frac{V_m^2}{2\pi} \left\{ \frac{\omega t}{2} - \frac{\sin 2\omega t}{4} \right\}_{wt=0}^{\pi}$$

$$V_{\text{out}}^2(\text{rms}) = \frac{V_m^2}{2\pi} \left\{ \left( \frac{\pi}{2} - \alpha \right) - \frac{\sin 2\alpha}{4} - \frac{\sin \alpha}{4} \right\}$$

$$V_{\text{out}}^2(\text{rms}) = \frac{V_m^2}{2\pi} \times \frac{\pi}{2} = \frac{V_m^2}{4}$$

$$V_{\text{out}}(\text{rms}) = \frac{V_m}{2}$$

$$I_{\text{out}}(\text{rms}) = \frac{I_m}{2}$$

$$I_m = \frac{V_m}{R_L}$$

c) Rectifier efficiency ( $\eta$ ): → It is the ratio of DC power at the o/p to the applied AC power

$$\% \eta = \frac{P_{\text{DC}}}{P_{\text{AC}}} \times 100$$

$$P_{\text{DC}} = V_{\text{dc}} I_{\text{dc}} = \frac{V_{\text{dc}}^2}{R_L} = I_{\text{dc}}^2 R_L$$

$$P_{\text{AC}} = V_{\text{out}}(\text{rms}) I_{\text{out}}(\text{rms}) = V_{\text{rms}} I_{\text{rms}} = \frac{V_{\text{rms}}^2}{R_L} = I_{\text{rms}}^2 R_L$$

$$P_{\text{DC}} = \frac{V_{\text{dc}}^2}{R_L} = \frac{\left(\frac{V_m}{2}\right)^2}{R_L} = \frac{V_m^2}{\pi^2 R_L} \quad \text{--- (a)}$$

$$P_{\text{AC}} = \frac{V_{\text{rms}}^2}{R_L} = \frac{\left(\frac{V_m}{2}\right)^2}{R_L} = \frac{V_m^2}{4 R_L} \quad \text{--- (b)}$$

$$\% \eta = \frac{P_{\text{DC}}}{P_{\text{AC}}} \times 100 = \frac{\frac{V_m^2}{\pi^2 R_L}}{\frac{V_m^2}{4 R_L}} \times 100$$

$$\% \eta = \frac{4}{\pi^2} \times 100$$

$$\% \eta = 40.56 \% \quad \text{HWR}$$

d) Ripple factor ( $r$ ):

It is the ratio of rms value of o/p AC component to the DC component of rectifier o/p

$$\gamma = \frac{I_{ac}}{I_{dc}}$$

$$I_{ac} = \sqrt{I_{out(m)s}^2 - I_{dc}^2}$$

i.e.  $\frac{I_{ac}}{I_{dc}} = \sqrt{\frac{I_{ms}^2}{I_{dc}^2} - 1}$

i.e. 
$$\gamma = \sqrt{\frac{I_{ms}^2}{I_{dc}^2} - 1}$$

For HWR,  $I_{ms} = \frac{I_m}{2}$ ,  $I_{dc} = \frac{I_m}{\pi}$

$$\gamma = \sqrt{\frac{\frac{I_m^2}{4}}{\frac{\pi^2}{4}} - 1} = \sqrt{\frac{\pi^2}{4} - 1}$$

$\gamma = 1.21$  <sub>HWR</sub>

— X —









