
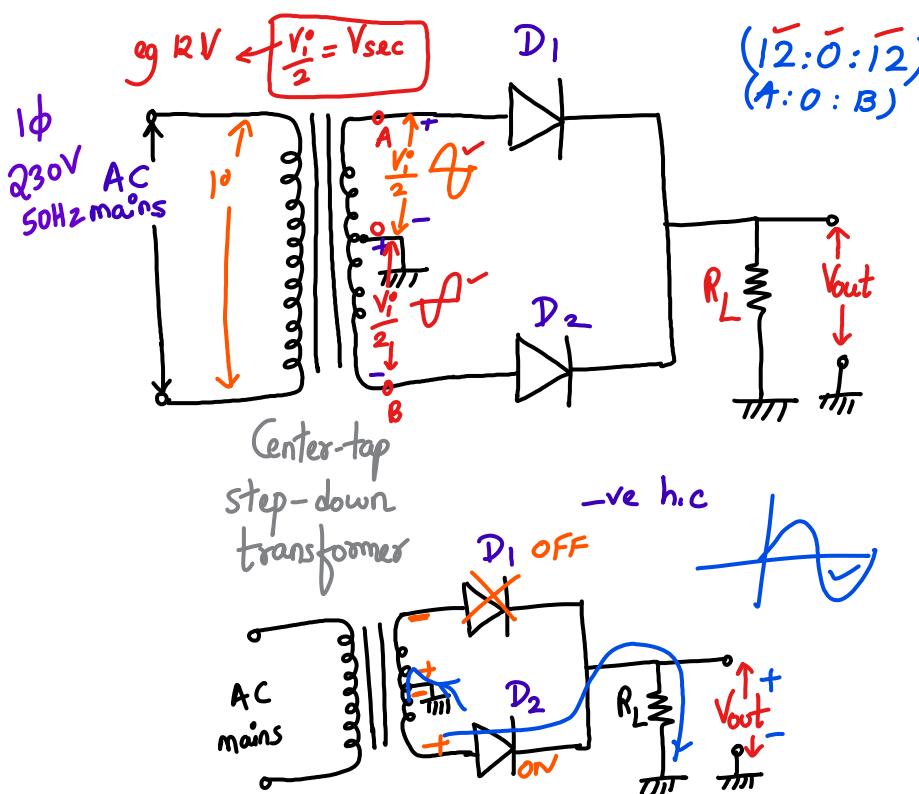


## # Full-wave rectifier with 'R' load:

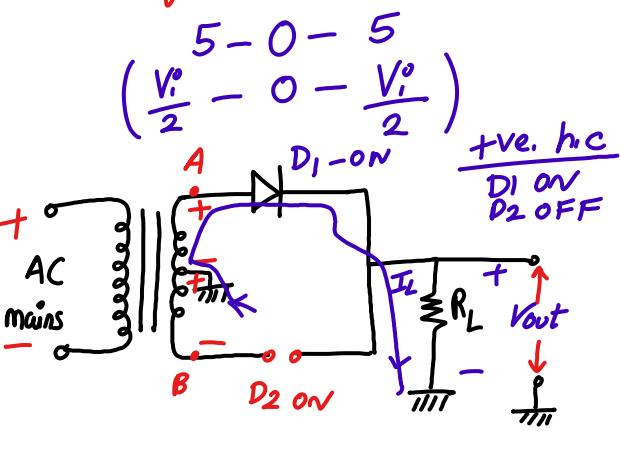


$V_i^o \Rightarrow$  Secondary voltage of transformer




$$V_{out} = \frac{V_i^o}{2} (\sqrt{m} \sin \omega t) \text{ if } 0 < \omega t < \pi$$

$$= \frac{V_i^o}{2} (\sqrt{m} \sin \omega t) \text{ if } \pi < \omega t < 2\pi$$


①

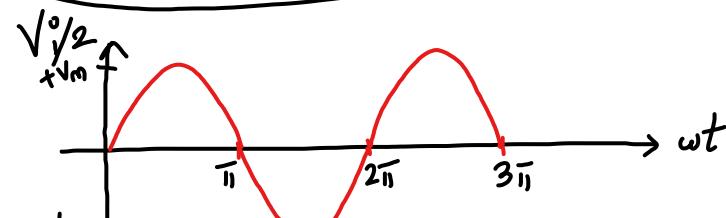

$$V_{out} = I_{out} R_L$$

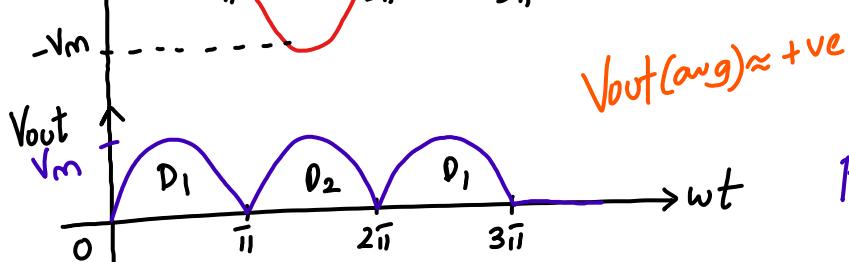

FWR I/P &  
O/P waveforms

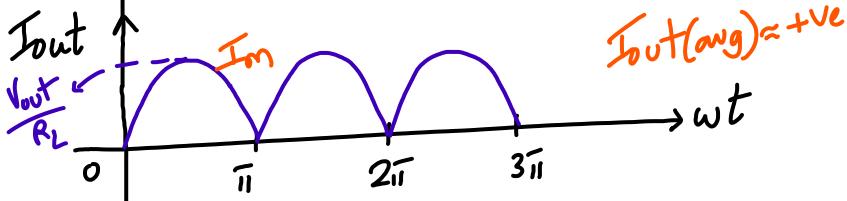

$I_m = \frac{V_m}{R_L}$

## FWR with 'R' load analysis:

- { Derive a) Expression for rectification efficiency ( $\eta$ ) }
- b) Expression for ripple factor ( $\gamma$ ) }
- c) Expression for TUF }

$$\textcircled{1} \quad V_{\text{out(avg)}} = V_{\text{dc}} = \frac{1}{T} \int_0^T V_{\text{out}} dt$$

i.e.  $V_{\text{dc}} = \frac{1}{\pi} \int_0^{\pi} v_i(\omega t) dt$

i.e.  $V_{\text{dc}} = \frac{1}{\pi} \left[ \int_0^{\pi} V_m \sin \omega t dt \right]$


i.e.  $V_{\text{dc}} = \frac{V_m}{\pi} [-\cos \omega t]_{\omega t=0}$

i.e.  $V_{\text{dc}} = \frac{V_m \times \{-[\cos \pi - \cos 0]\}}{\pi} = \frac{V_m}{\pi} \times -1 \times (-2)$


i.e.  $V_{\text{dc}} = \frac{2V_m}{\pi}$

FWR

$V_{\text{out(avg)}}$

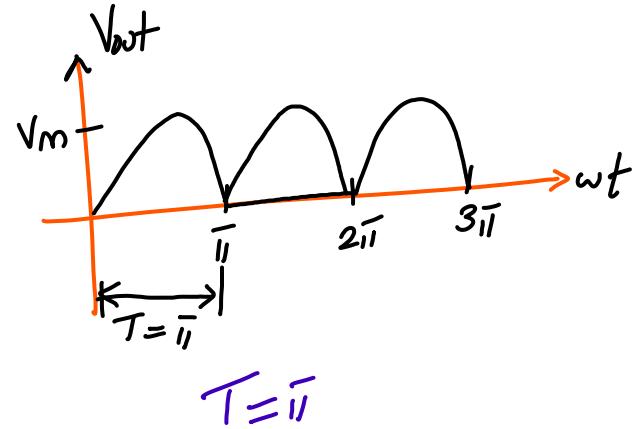

$$T = \pi$$

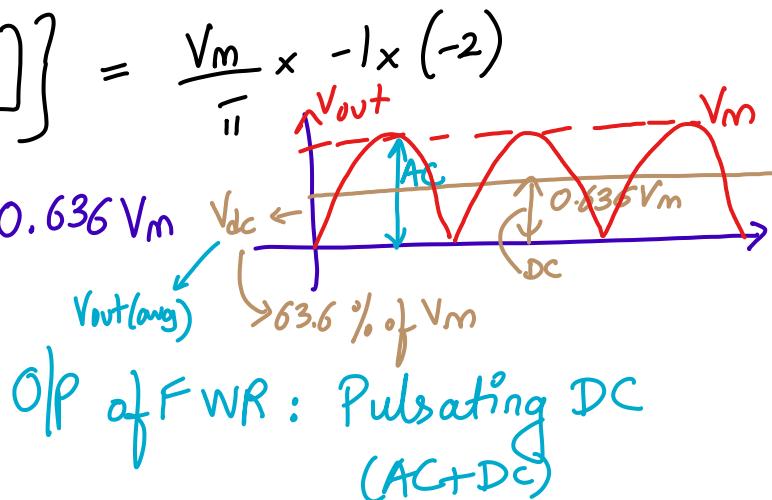

$$V_{\text{out(avg)}} = V_{\text{dc}} = \frac{2V_m}{\pi}$$

$$\textcircled{2} \quad I_{\text{out(avg)}} = \frac{V_{\text{out(avg)}}}{R_L} = \frac{V_{\text{dc}}}{R_L} = \frac{2V_m}{\pi R_L} \xrightarrow{\text{Im}} \left( V_{\text{out(avg)}} = I_{\text{out(avg)}} R_L \right)$$

$$I_{\text{out(avg)}} = \frac{2 \text{Im}}{\pi}$$

where,  $\boxed{\text{Im} = V_m/R_L}$

$$I_{\text{out(avg)}} = I_{\text{dc}}$$

\textcircled{3}  $V_{\text{out(rms)}}$   $\rightarrow$  RMS value of AC component of output

$$V_{\text{out(rms)}} = \left[ \frac{1}{T} \int_0^T V_{\text{out}}^2(wt) dwt \right]^{1/2}$$

$$\text{i.e } V_{\text{out(rms)}} = \left[ \frac{1}{\pi} \int_0^{\pi} V_i^2(wt) dwt \right]^{1/2}$$

$$\bar{T} = \pi$$

For m eq^n \textcircled{1},

$$\text{i.e } V_{\text{out(rms)}} = \left[ \frac{1}{\pi} \left\{ \int_0^{\pi} V_m^2 \sin^2 wt dwt \right\} \right]^{1/2}$$

$$\text{i.e } V_{\text{out(rms)}} = \left[ \frac{V_m^2}{\pi} \left\{ \int_0^{\pi} \left( 1 - \frac{\cos 2wt}{2} \right) dwt \right\} \right]^{1/2}$$

$$\sin^2 x = \frac{1 - \cos 2x}{2}$$

$$\text{i.e } V_{\text{out(rms)}} = \left[ \frac{V_m^2}{2\pi} \left\{ \left. wt - \frac{\sin 2wt}{2} \right|_{wt=0}^{\pi} \right\} \right]^{1/2}$$

$$\text{i.e } V_{\text{out(rms)}} = \left[ \frac{V_m^2}{2\pi} \left\{ (\pi - 0) - \frac{\sin 2\pi}{2} - \frac{\sin 0}{2} \right\} \right]^{1/2}$$

$$\text{i.e } V_{\text{out(rms)}} = \left[ \frac{V_m^2}{2\pi} \times \pi \right]^{1/2} = \left( \frac{V_m^2}{2} \right)^{1/2}$$

$$\text{i.e } V_{\text{out(rms)}} = \frac{V_m}{\sqrt{2}}$$

FWR

where,

$$I_{\text{out rms}} = \frac{\text{Im}}{\sqrt{2}}$$

$$\boxed{\text{Im} = \frac{V_m}{R_L}}$$

$$V_{\text{out(rms)}} = V_{\text{rms}} ; I_{\text{out rms}} = I_{\text{rms}}$$

#### ④ Rectification efficiency ( $\eta$ ):

$$\% \eta = \frac{P_{DC}}{P_{AC}} \times 100$$

It is the ratio of DC power at the output to the applied input AC power

$$P_{DC} = V_{dc} I_{dc} = \frac{V_{dc}^2}{R_L} = \overline{I_{dc}^2} R_L$$

$$P_{AC} = V_{rms} I_{rms} = \frac{V_{rms}^2}{R_L} = \overline{I_{rms}^2} R_L$$

$$\text{ie } P_{DC} = \frac{V_{dc}^2}{R_L} = \frac{\left(\frac{2V_m}{\pi}\right)^2}{R_L} = \frac{4V_m^2}{\pi^2 R_L} \quad - (a)$$

$$\text{ie } P_{AC} = \frac{V_{rms}^2}{R_L} = \frac{\left(\frac{V_m}{\sqrt{2}}\right)^2}{R_L} = \frac{V_m^2}{2 R_L} \quad - (b)$$

$$\text{ie } \% \eta = \frac{P_{DC}}{P_{AC}} \times 100 = \frac{\frac{4V_m^2}{\pi^2 R_L}}{\frac{V_m^2}{2 R_L}} \times 100 = \frac{8}{\pi^2} \times 100$$

i.e.  $\% \eta = \frac{8}{\pi^2} \times 100 \approx 81.05 \%$

Rectification efficiency of FWR with  $R'$  load

\*  $\eta_{FWR} > \eta_{HWR}$

## ⑤ Ripple factor ( $\gamma$ ):

It is the ratio of rms value of AC component to the DC component of the rectifier output

Smaller the AC component  $\rightarrow$  more effective is the rectifier

$$\gamma = \frac{I_{ac}}{I_{dc}} = \frac{V_{ac}}{V_{dc}}$$

$$; I_{ac} = \sqrt{I_{out(rms)}^2 - I_{dc}^2}$$

Remember it!

$$ie \frac{I_{ac}}{I_{dc}} = \sqrt{\frac{I_{rms}^2}{I_{dc}^2} - 1}$$

$$ie \gamma = \sqrt{\frac{I_{rms}^2}{I_{dc}^2} - 1}$$

$$I_{out(rms)}^2 = I_{rms}^2$$

$$For FWR, I_{rms} = \frac{Im}{\sqrt{2}}, I_{dc} = \frac{Im \times 2}{\pi}$$

$$\gamma = \sqrt{\frac{\frac{Im^2}{2}}{\frac{4 \cdot \frac{Im^2}{\pi^2}}{\pi^2}} - 1} = \sqrt{\frac{\pi^2}{4} - 1}$$


$$\gamma = \sqrt{\frac{\pi^2}{8} - 1} \approx 0.483$$

Fwctr

$$\gamma_{FWR} < \gamma_{HWR}$$

$\hookrightarrow$  contains smaller ac component

# # Full-wave Bridge rectifier

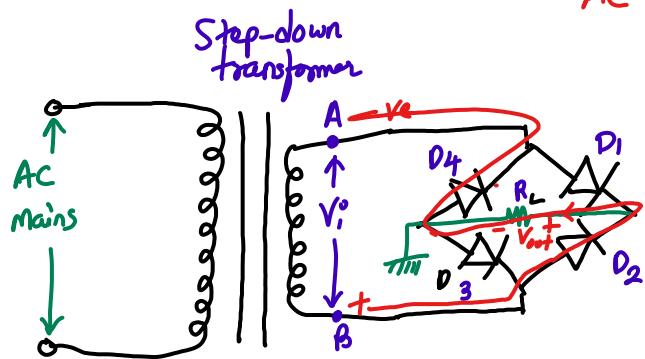

+ve h.c. of  $V_i^o \rightarrow D_1 \& D_3 \rightarrow ON$   
 $I_{out} \rightarrow A - D_1 - R_L - D_3 - B - A$

-ve h.c. of  $V_i^o \rightarrow D_2 \& D_4 \rightarrow ON$   
 $I_{out} \rightarrow B - D_2 - R_L - D_4 - A$   
 +ve during -ve h.c. also

