

Course Name:	Digital Design Laboratory	Semester:	III
Date of Performance:	___ / ___ / ____	Batch No:	E2
Faculty Name:		Roll No:	16010123325
Faculty Sign & Date:		Grade/Marks:	___/25

Experiment No: 5
Title: Flip Flops

Aim and Objective of the Experiment:

To Verify truth table of JK Flip flop using IC 7476 and study conversion of JK FF to D FF and T FF

COs to be achieved:

CO3: Design synchronous and asynchronous sequential circuits.

Tools used:

Trainer kits

Theory:

Flip-flop is the common name given to two-state devices which offer basic memory for sequential logic operations. Flip-flops are heavily used for digital data storage and transfer and are commonly used in banks called "registers" for the storage of binary numerical data.

JK-flip flop: has two inputs, traditionally labeled J and K. IC 7476 is a dual JK master slave flip flop with preset and clear inputs. If J and K are different then the output Q takes the value of J at the next clock edge. If J and K are both low then no change occurs. If J and K are both high at the clock edge, then the output will toggle from one state to the other. It can perform the functions of the set/reset flip-flop and has the advantage that there are no ambiguous states.

D Flip Flop: tracks the input, making transitions with match those of the input D. The D stands for "data"; this flip-flop stores the value that is on the data line. It can be thought of as a basic memory cell. D flip-flop can be made from J-K flip-flop by connecting both inputs through a not gate.


T Flip Flop: T or "toggle" flip-flop changes its output on each clock edge, giving an output which is half the frequency of the signal to the T input. It is useful for constructing binary counters, frequency dividers, and general binary addition devices. It can be made from a J-K flip-flop by tying both of its inputs high.

Implementation Details:


Procedure

- 1) Locate IC 7476 on Digital trainer kit
- 2) Apply various inputs to J & K pins by means of the output on logic output indicator.
- 3) Connect a pulsar switch to the clock input.
- 4) Connect the J&K as D and T flip flop as shown in diagrams and verify the respective truth tables.

Logic Symbol

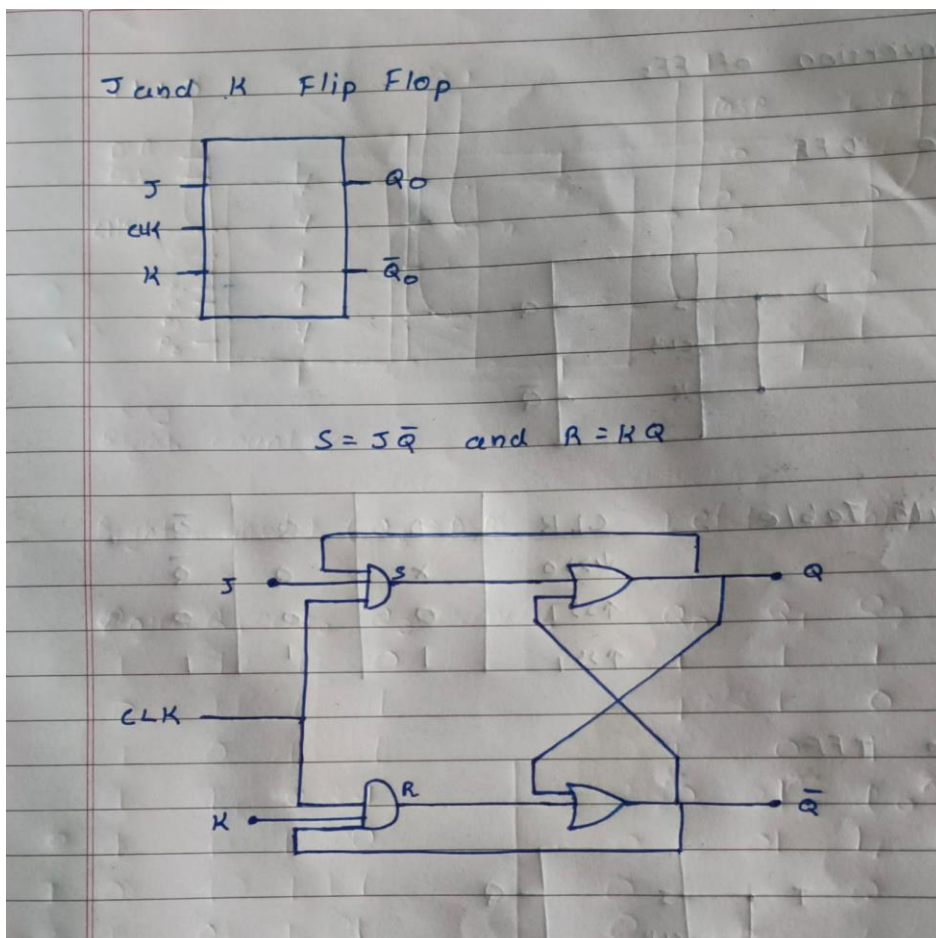

Pin Diagram of IC 7476

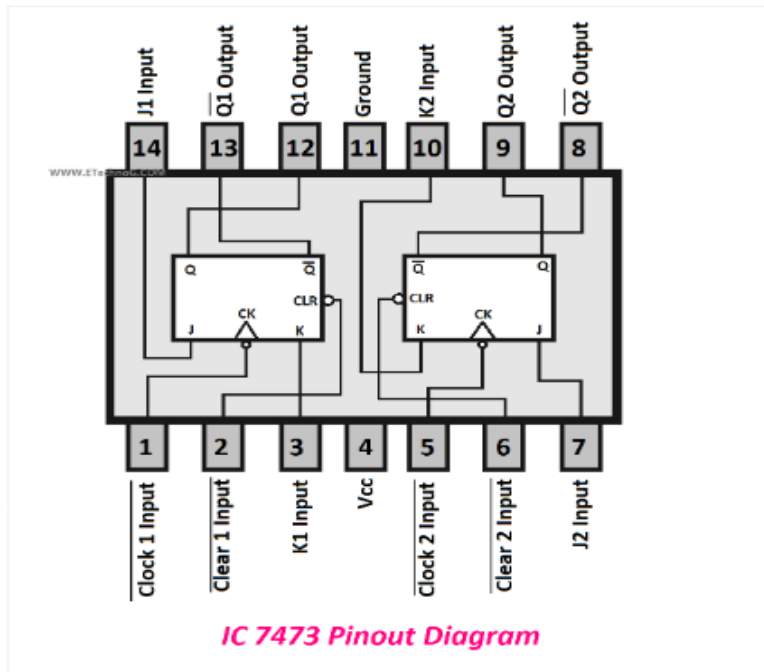

Truth Table of JK FF


CLK	J	K	PR	CLR	Q	BAR(Q)
X	X	X	0	1	1	0
X	X	X	1	0	0	1
↑	0	0	1	1	Q	Q
↑	0	1	1	1	0	1
↑	1	0	1	1	1	0
↑	1	1	1	1	Q	Q



Conversion of FFs

conversion of FFs


1) To DFF

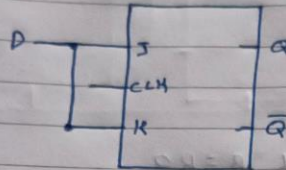

Truth Table :

CLK	D	Q	\bar{Q}
$\downarrow \gg 0$	x	Q	\bar{Q}
$\uparrow \gg 1$	0	0	1
$\uparrow \gg 1$	1	1	0

2) To TFF

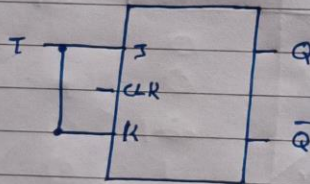

Truth Table :

T	Previous		Next	
	Q	\bar{Q}	Q	\bar{Q}
0	0	1	0	1
0	1	0	1	0
1	0	1	1	0
1	1	0	0	1

Implementation Details

Procedure:

- 1) Locate the IC 7476 and place the IC on trainer kit.
- 2) Connect VCC and ground to respective pins of IC trainer kit.
- 3) Implement the circuit as shown in the circuit diagram.
- 4) Connect the inputs to the input switches provided in the trainer kit.
- 5) Connect the outputs to the switches of O/P LEDs
- 6) Apply various combinations of inputs according to the truth table and observe the condition of LEDs.
- 7) Note down the corresponding output readings for various combinations of inputs.

Post Lab Subjective/Objective type Questions:

1. How does a JK flip-flop differ from an SR flip-flop in its basic operation?

JK Flip-Flop: Can toggle its output; has inputs J (set) and K (reset) with states: No Change, Reset, Set, or Toggle.

SR Flip-Flop: Can only set or reset; has inputs S (set) and R (reset) with states: No Change, Set, or Reset.

2. What is the use of characteristic and excitation table?

Characteristic Table: Shows the relationship between flip-flop inputs and outputs for each state transition.

Excitation Table: Helps determine the necessary inputs to achieve a desired state transition in a flip-flop.

3. How many flip flops do you require storing the data 1101?

You need 4 flip-flops to store the 4-bit binary data 1101. Each flip-flop stores one bit.

4. Virtual Lab for Flipflop. Perform Simulation give feedback.

<https://de-iitr.vlabs.ac.in/exp/truth-tables-flip-flops/simulation.html>

Conclusion:

We verified the JK flip-flop truth table using IC 7476 and explored converting JK flip-flops to D and T flip-flops.

Signature of faculty in-charge with Date: