

# Diodes

## \* Introduction to semi-conductors


- Silicon & Germanium are two types of semiconducting materials.  
Both have 'four' valence electron.
  - Intrinsic crystal is one that has no impurities.
  - Doping is the process of adding impurities to intrinsic semiconducting materials to increase & control conductivity within the material.
- n-type is formed by adding pentavalent (5 valence electrons) impurity atoms  
eg:- Ph, As, Sb
- electrons are called majority carriers in n-type material.
  - holes are minority carriers in n-type material.
- p-type material is formed by adding trivalent (3 valence e<sup>-</sup>) impurity atoms  
eg:- B, Ga, In, Al
- holes are called majority carriers in p-type material.
  - electrons are called minority carriers in p-type material.

## \* P-N Junction

- It is formed by joining p-type & n-type semiconductors.
- 'Junction' refers to boundary interface where the two regions of the semiconductor meet.
- It is created in a single crystal of semiconductor by doping by ion implantation / diffusion of dopants / epitaxy (growing a layer of crystal doped with one type of dopant on top of a layer of crystal doped with another type of dopant).
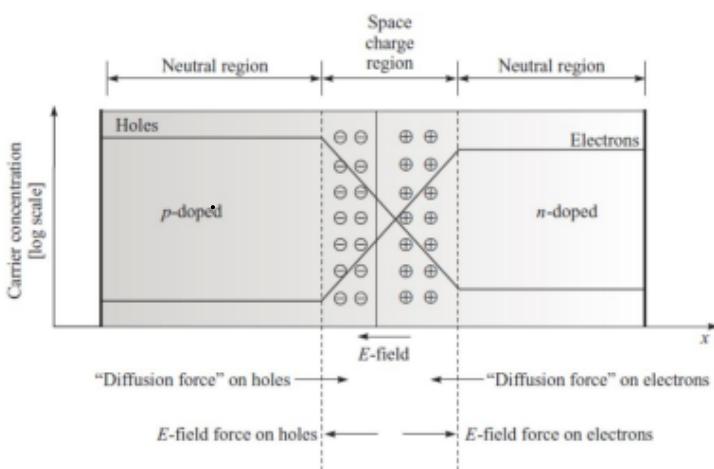
### \* P-n junc in thermal equilibrium: with zero bias voltage applied.

- The region nearby the p-n interfaces lose their neutrality and become charged, forming the space charge region or depletion layer.



- The electric field created by the space charge region opposes the diffusion process for both electrons & holes.

- There are two concurrent phenomena. the diffusion process that tends to generate more space charge, and the electric field generated by the space charge that tends to counteract the diffusion.

- The space charge region is a zone with a net charge provided by the fixed ions (donors or acceptors) that have been left uncovered by majority carrier diffusion
- When equilibrium is reached, the charge density is approximated by the displayed step func".
- The region is completely depleted of majority carriers (leaving a charge density equal to the net doping level), and the edge between the space charge region is quite sharp.
- The space charge has the same charge on both sides of the p-n interfaces, thus it extends farther on the less doped side.

### Energy band diagram of PN Junction (under equilibrium)

i) Depletion region width ( $w$ ):

$$w = \sqrt{\frac{2 \epsilon_s}{q} V_{bi} \left( \frac{N_A + N_D}{N_A N_D} \right)} \text{ cm}$$

ii) Build-in E-field ( $E_{\text{build-in}}$ )

$$E_{\text{build-in}} = - \frac{2 V_{bi}}{w} \frac{V}{\text{cm}}$$

responds

iii) Built-in potential ( $V_{bi}$ )

$$V_{bi} = \frac{kT}{q} \ln \left( \frac{N_A N_D}{n_i^2} \right) \text{ Volts}$$

## \* Forward biasing of p-n junction

- External voltage applied to the junction in such a direction that it cancels the potential barrier, thus permitting current flow is called forward biasing.
- For this, connect +ve terminal of battery to p-type & -ve terminal to n-type.
- The applied forward potential establishes the electric field which acts against the field due to potential barrier. Therefore, the resultant field is weakened and the barrier height is reduced at the junc".
- ∵ the potential barrier voltage is small, a small forward voltage is sufficient to completely eliminate the barrier.
- Once the potential barrier is eliminated by the forward voltage, junc" resistance becomes almost zero and a low resistance path is established for the entire circuit.  
∴ current flows in the circuit. This is called forward current.

## \* Reverse biasing of p-n junction

- External voltage applied to the junc is in such a direction the potential barrier is increased it is called reverse biasing.
- For this, connect -ve terminal of the battery to p-type & +ve terminal to n-type.
- The applied reverse voltage establishes an electric field which acts in the same direction as the field due to potential barrier. Therefore, the resultant at the junc is strengthened & the barrier height is increased.
- The increased potential barrier prevents the flow of charge carrier across the junc. Thus, a high resistance path is established for the entire circuit & hence current does not flow.

## \* VI characteristics of P-N junc diode

\* I-V relationship in a PN junction diode / diode eqn.

$$I_D = I_s \left( e^{\frac{V_D}{nV_T}} - 1 \right)$$

where,  $I_D$  is diode current in mA

$V_D$  is applied diode voltage in volts

$I_s$  is leakage or reverse saturation <sup>current</sup>

$n$  is ideality factor ( $n_{Ge} = 1.4$  &  $n_{Si} = 2$ )

$V_T$  is thermal voltage at  $T = 300\text{K}$

$$V_T = \frac{kT}{q} = \frac{T}{11600}; V_T = 26\text{mV}, T = 300\text{K}$$

↳ Shockley's eqn

Diode current eqn

With zero voltage :-

$$V_D = 0, \therefore I_D = I_s \left( e^{\frac{V_D}{nV_T}} - 1 \right) = I_s (e^0 - 1) = 0$$

Forward biased :-

$$V_D > 0$$

When  $V_D \gg nV_T$  then,


$$e^{\frac{V_D}{nV_T}} \gg 1 \quad \& \quad I_D \approx I_s e^{\frac{V_D}{nV_T}}$$

Reversed - biased:


$$V_D < 0$$

When  $V_D \ll nV_T$  then,
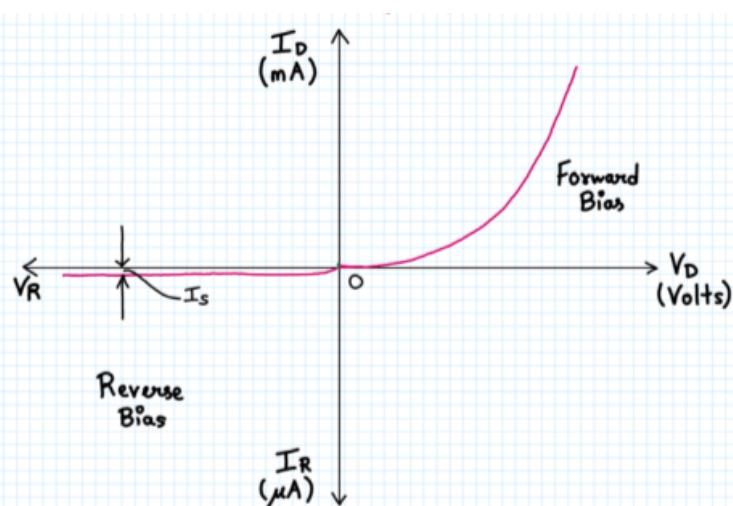
$$e^{\frac{V_D}{nV_T}} \ll 1 \quad \& \quad I_D \approx -I_s \quad \text{i.e. reverse current saturates to } I_s \text{ in reverse direction.}$$




I-V characteristics of diode

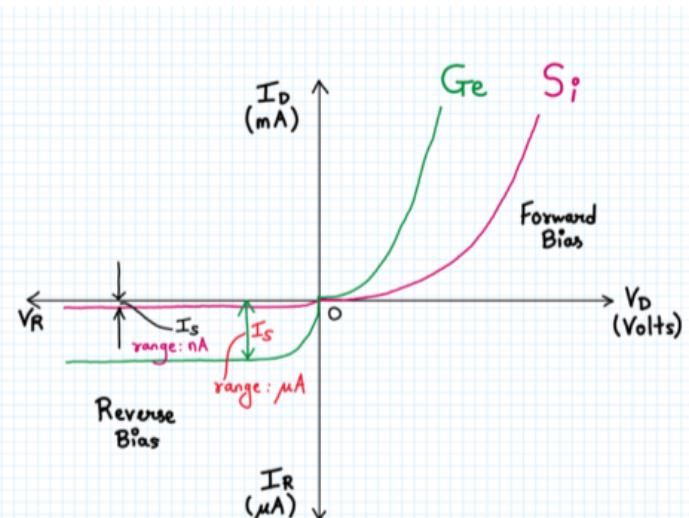


I-V characteristics of Si and Ge diode
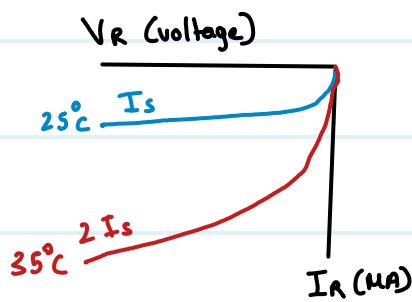
## \* Temp dependence on diode I-V characteristics

- $V_T$  &  $I_S$  in diode eqn are temp dependent terms.
- ↑ in temp results in ↑ thermal activity and ↓ diode resistance, which influences both the forward & reverse characteristics of diode.
- Diode forward voltage decreases by 2.5 mV per degree rise in temp.



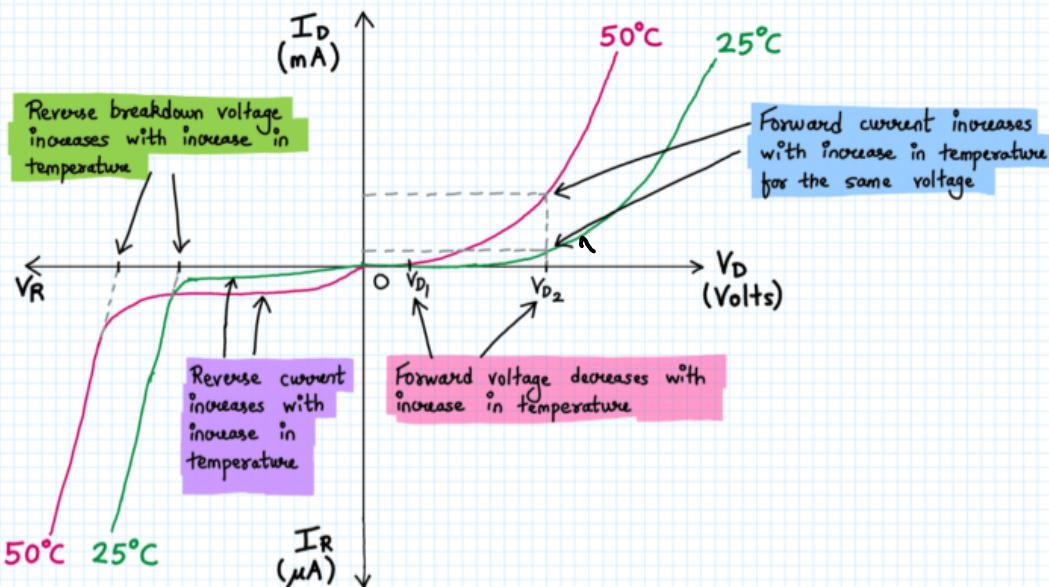- Reverse saturation current & breakdown voltage ↑ with ↑ in temp.
- Reverse saturation current gets doubled for every  $10^\circ\text{C}$  rise in temp



**Effect of temperature on the diode characteristics**

### Q] \* Numerical 1

Find the forward current in a Si diode at a forward voltage of 0.6V, reverse saturation current of 0.1μA and temperature of  $27^\circ\text{C}$

$$V_D = 0.6\text{V}, I_s = 0.1\mu\text{A}, V_T = 26\text{mV} \quad I_D = ?$$

Now, if a reverse voltage of 10V is applied to the diode  $\eta = \gamma_i = 2$

Find the reverse current flowing through the diode

→ Diode eqn is

$$I_D = I_s \left( e^{\frac{V_D}{\eta V_T}} - 1 \right)$$

$$T = 27^\circ\text{C} = 300\text{K}$$

For Si,  $\eta = 2$  &  $V_T \approx 26\text{mV}$  at  $T = 27^\circ\text{C}$

$$\frac{V_D}{\eta V_T} = \frac{0.6}{2 \times 26\text{mV}} = x_1 = 11.53$$

$$I_D = 0.1 \times 10^{-6} \left( e^{11.53} - 1 \right)$$

$$I_D = x_2 = 10.172 \text{ mA}$$

∴  $I_D \approx x_2$  ..... Forward current in a Si diode

$$\rightarrow V_D = -10\text{V};$$

$$I_D = I_s \left( e^{\frac{-10}{2 \times 26\text{mV}}} - 1 \right)$$

$$I_D = I_s (x_3 - 1) \quad e^{-192.36} \approx 0 \approx x_3$$

$$\therefore I_D = -I_s = -0.1 \times 10^{-6}$$

∴  $I_D = -0.1\text{mA} = x_4$  ..... Reverse current in Si diode

Q]

## \* Numerical 2

The reverse saturation current of a Ge diode at 27°C is  $5\mu A$

Find the forward voltage at which the current is 25 mA

→ Given,

$$T = 27^\circ C = 300 K, I_s = 5 \text{ mA}, I_D = 25 \text{ mA}, \eta = 1 (\text{Ge}), V_T = 26 \text{ mV}$$

$$I_D = I_s \left( e^{\frac{V_D}{\eta V_T}} - 1 \right)$$

$$I_D + I_s = I_s e^{\frac{V_D}{\eta V_T}}$$

$$e^{\frac{V_D}{\eta V_T}} = 1 + \frac{I_D}{I_s} = 1 + \frac{25 \times 10^{-3}}{5 \times 10^{-6}}$$

$$e^{\frac{V_D}{\eta V_T}} = 500 \cdot 1 = 500$$


$$\frac{V_D}{\eta V_T} = \ln(500) = 8.517$$

$$V_D = 8.517 \times 26 \times 10^{-3}$$

$$V_D = 0.221 \text{ V} \quad \dots \dots \text{ Forward voltage of Ge diode}$$

## ★ Diode Applications:-

### 1] Rectifier

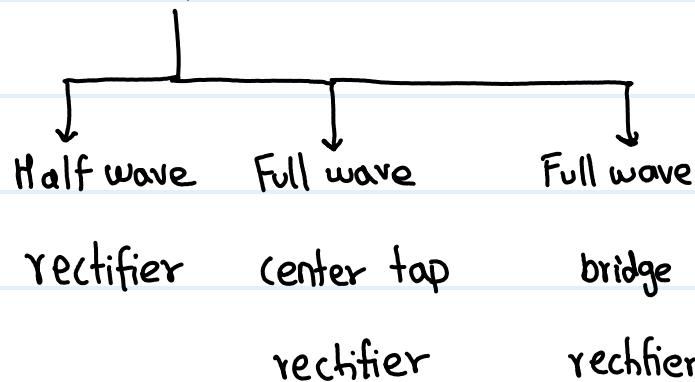

① CKT diag<sup>n</sup>

② working



③ I/p - O/p w.r.t time

④ Analysis:-

- a)  $V_{out}$  (avg) {  $I_{out}$  avg }
- b)  $V_{out}$  (rms) {  $I_{out}$  rms }
- c) Rectification eff (%)
- d) Ripple factor (%)
- e) TUF


### # Half-wave Rectifier with 'R' load:

Circuit diagram:-

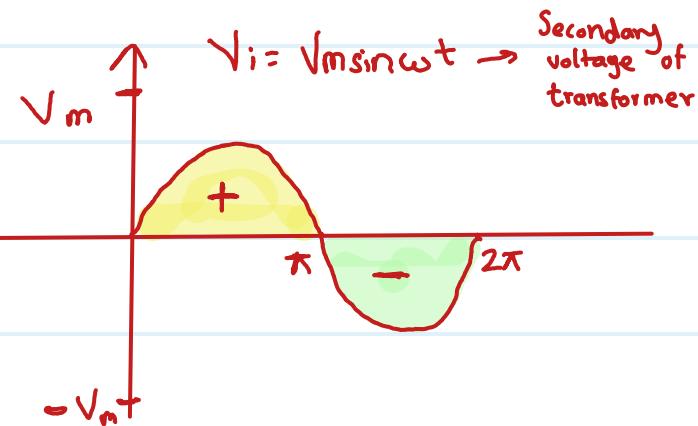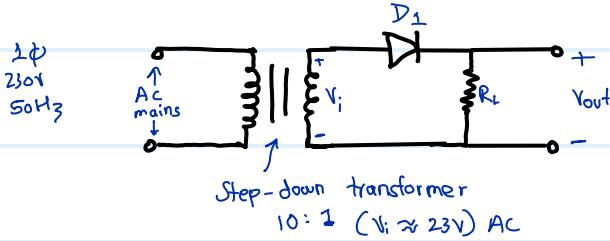


Case I: During +ve half cycle of  $x_p(V_i)$

$D_1$  is F.B i.e ON

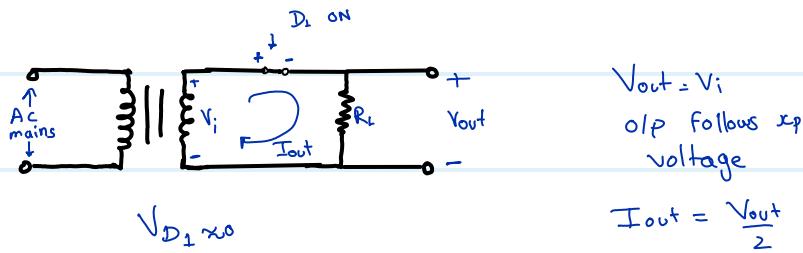

Case II: During -ve half cycle of g/p ( $V_i$ )

$D_L$  is R.B i.e OFF

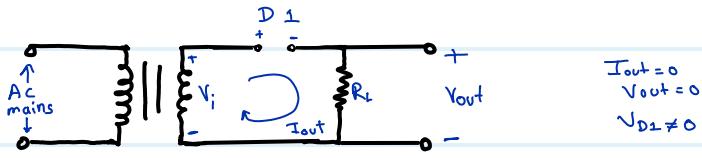


$$\begin{aligned} I_{out} &= 0 \\ V_{out} &= 0 \\ V_{D_L} &\neq 0 \end{aligned}$$

("PIV rating")

Input - output wlf's:-
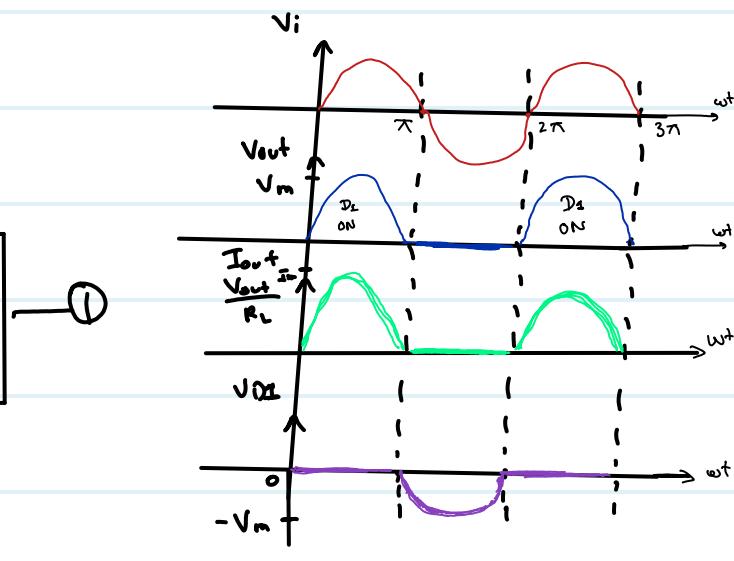
$$\begin{aligned} V_{out} &= V_i (\sqrt{2} \sin \omega t) \quad \text{if } 0 < \omega t < \pi \\ &= 0 \quad \text{if } \pi < \omega t < 2\pi \end{aligned}$$



Analysis :- HWR

a)

$$V_{out} = \frac{V_m}{\pi} \quad \left[ \text{i.e. } V_{DC} = 0.318 V_m \right]$$

$$I_{out} = \frac{I_m}{\pi}$$

b)

$$V_{out} = \frac{V_m}{2}, \quad I_{rms} = \frac{I_m}{2}$$

c)

Rectification efficiency ( $\eta$ ):  $\rightarrow \eta$  is ratio of DC power at the O/P to the applied I/P AC power

$$\eta = \frac{P_{DC}}{P_{AC}} \times 100$$

$$P_{DC} = V_{DC} I_{DC} = \frac{V_{DC}^2}{R_L} = I_{DC}^2 R_L$$

$$P_{AC} = V_{rms} I_{rms} = \frac{V_{rms}^2}{R_L} = I_{rms}^2 R_L$$

$$P_{DC} = \frac{V_{DC}^2}{R_L} = \frac{\left(\frac{V_m}{\pi}\right)^2}{R_L} = \frac{V_m^2}{\pi^2 R_L} \dots \textcircled{a}$$

$$P_{AC} = \frac{V_{rms}^2}{R_L} = \frac{\left(\frac{V_m}{2}\right)^2}{R_L} = \frac{V_m^2}{4R_L} \dots \textcircled{b}$$

$$\% \eta = \frac{P_{DC}}{P_{AC}} \times 100 = \frac{\frac{V_m^2}{\pi^2 R_L}}{\frac{V_m^2}{4R_L}} \times 100$$

$$\% \eta = \frac{4}{\pi^2} \times 100$$

$$\% \eta = 40.56 \% \text{ HWR}$$

d) Ripple factor ( $r$ ): It is ratio of rms value of o/p AC component to

the DC component

$$r = \frac{I_{AC}}{I_{DC}} \quad I_{AC} = \sqrt{I_{out(rms)}^2 - I_{DC}^2}$$

$$\text{i.e. } \frac{I_{AC}}{I_{DC}} = \sqrt{\frac{I_{rms}^2}{I_{DC}^2} - 1}$$

$$\therefore r = \sqrt{\frac{I_{rms}^2}{I_{DC}^2} - 1}$$

of rectifier o/p

$$\text{For HWR, } I_{rms} = \frac{I_m}{2}, I_{DC} = \frac{I_m}{\pi}$$

$$r = \sqrt{\frac{\frac{I_m^2}{4}}{\frac{I_m^2}{\pi^2}} - 1} = \sqrt{\frac{\pi^2}{4} - 1}$$

$$r = 1.21 \text{ HWR}$$

e) Transformer utilization factor: TUF is a quantitative indication of the utilization of VA rating of transformer. The more the value of TUF, the more will be the utilization. In other words, the VA rating of required transformer will be less if TUF is more & vice-versa

$$TUF = \frac{\text{DC Power Output}}{\text{Effective VA rating of transformer}} = \frac{P_{dc}}{\text{Effective VA rating of transformer}}$$


$$P_{dc} = I_{avg} \times V_{avg}$$

$$\therefore P_{dc} = \frac{V_m}{\pi} \times \frac{I_m}{\pi} \quad \text{--- } \textcircled{1}$$


$$\text{VA rating} = \frac{V_m}{\sqrt{2}} \times \frac{I_m}{2} \quad \text{--- } \textcircled{2}$$

$$\therefore TUF = \frac{P_{dc}}{\text{VA rating}} = \frac{2\sqrt{2}}{\pi^2} = 0.285$$
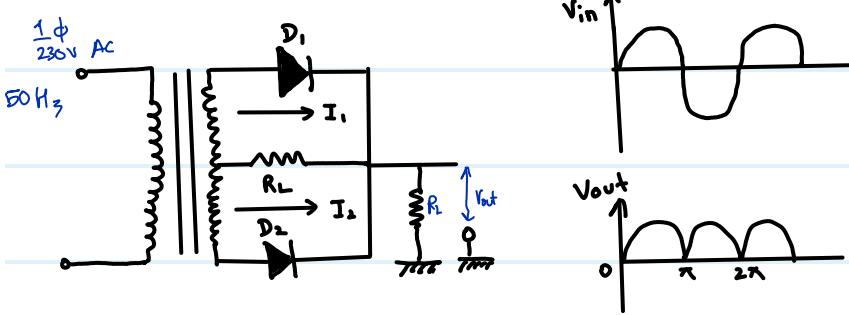
# Full wave "Center tapped" rectifier with 'R' load.



Full wave Bridge Rectifier

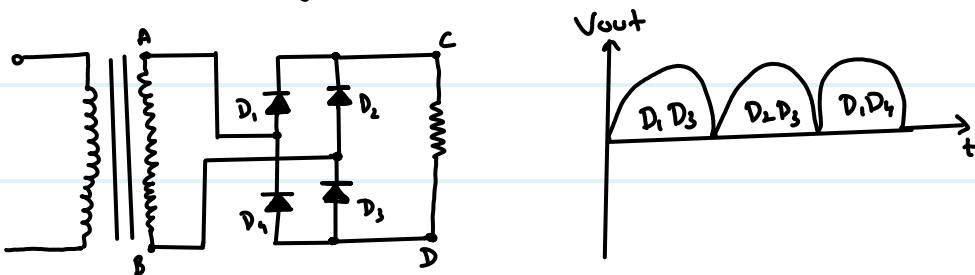

$$\textcircled{1} \quad V_{out(\text{avg})} = V_{dc} = 2 \frac{V_m}{\pi}$$

$$\textcircled{2} \quad I_{out(\text{avg})} = \frac{V_{avg}}{R_L} = \frac{2 I_m}{R_L}$$

$$\textcircled{3} \quad V_{out(\text{rms})} = \frac{V_m}{\sqrt{2}}, \quad I_{rms} = \frac{I_m}{\sqrt{2}}$$

$$\textcircled{4} \quad \eta = \frac{8}{\pi^2} \times 100 \approx 81.05 \%$$

$$\eta_{FWR} > \eta_{HWR}$$

$$\textcircled{5} \quad \text{Ripple factor } (\gamma) = \sqrt{\frac{\pi^2 - 1}{8}} = 0.483 \quad \gamma_{FWR} < \gamma_{HWR}$$

⑥

$$TUF = 0.672 \text{ FWCTR}$$

$$TUF = 0.816 \text{ FWBR}$$

$\therefore$  Comparisons of Rectifiers

| Particulars       | HWR               | FWCTR                  | FWBR                   |
|-------------------|-------------------|------------------------|------------------------|
| ① No. of diodes   | 1                 | 2                      | 4                      |
| ② $I_{dc}$        | $\frac{I_m}{\pi}$ | $\frac{2I_m}{\pi}$     | $\frac{2I_m}{\pi}$     |
| ③ $\sqrt{V_{dc}}$ | $\frac{V_m}{\pi}$ | $\frac{2V_m}{\pi}$     | $\frac{2V_m}{\pi}$     |
| ④ $I_{rms}$       | $\frac{I_m}{2}$   | $\frac{I_m}{\sqrt{2}}$ | $\frac{I_m}{\sqrt{2}}$ |
| ⑤ $\eta$          | 40.6%             | 81.2%                  | 81.2%                  |
| ⑥ PIV             | $V_m$             | $2V_m$                 | $V_m$                  |
| ⑦ Ripple factor   | 1.21              | 0.48                   | 0.48                   |
| ⑧ TUF             | 0.285             | 0.672                  | 0.812                  |