

EEEEE BJT CE configuration

12/11/23

- most famous configuration for BJT as amplifier


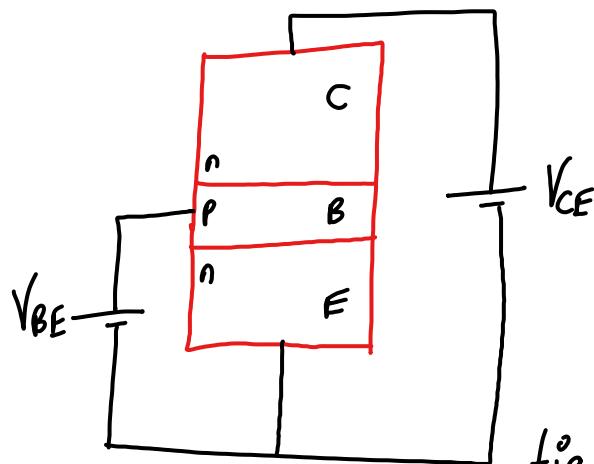
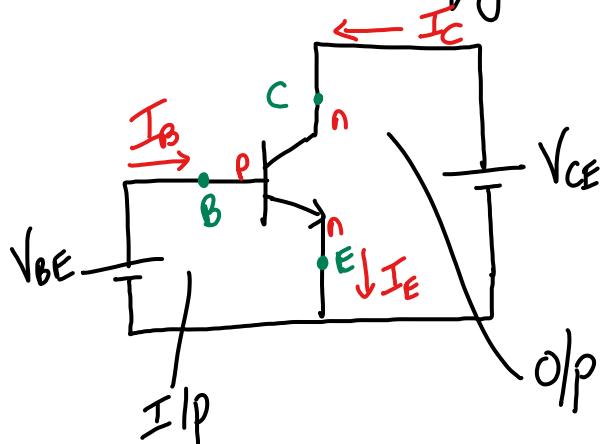


fig 1

npn BJT in
active region → BE Jⁿ F.B
BC Jⁿ R.B

① Input characteristics:

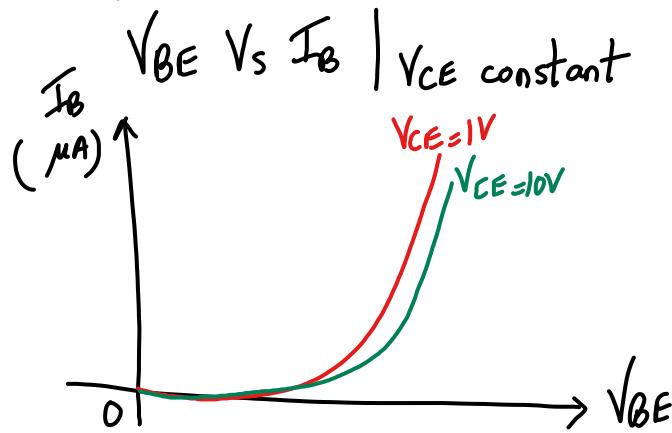

② I_p characteristics is similar to PN Jⁿ characteristics since BE Jⁿ is forward-biased
i.e As V_{BE} ↑, I_B ↑ is exponentially for constant V_{CE} value
(i.e BC Jⁿ is R.B)

③ As V_{CE} ↑ is → I_B is reducing? Why?

a) $V_{CE} = V_{CB} + V_{BE}$ ($V_{CB} = V_{CE} - V_{BE}$)


∴ with V_{BE} constant, if V_{CE} ↑ → V_{CB} ↑ is emitter is common terminal

b) As V_{CB} ↑, CB Jⁿ is more R.B



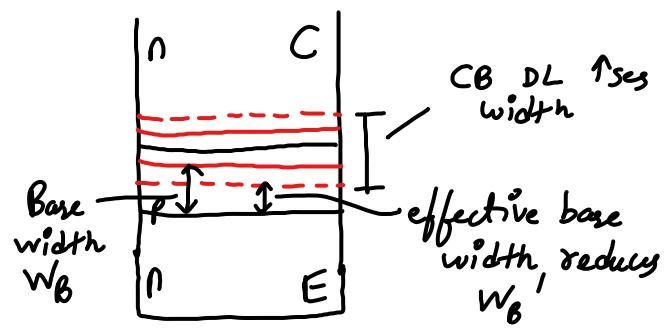c) i.e. CB depletion region width \uparrow V_{CE}

i.e. effective base width reduces from W_B to W_B'



d) i.e. possibility of e^- -holes recombination in base region will reduce

e) i.e. Most of e^- s travelling from emitter to base gets collected at collector.


i.e. I_B reduces

\therefore As $V_{CE} \uparrow$ $\downarrow I_B$ i.e. curve shifts left hand side


④ Input resistance from input characteristics (CE config)

$$R_{in} = \frac{\Delta V_{BE}}{\Delta I_B} \quad | \quad V_{CE} \text{ constant}$$

large value (in $M\Omega$)

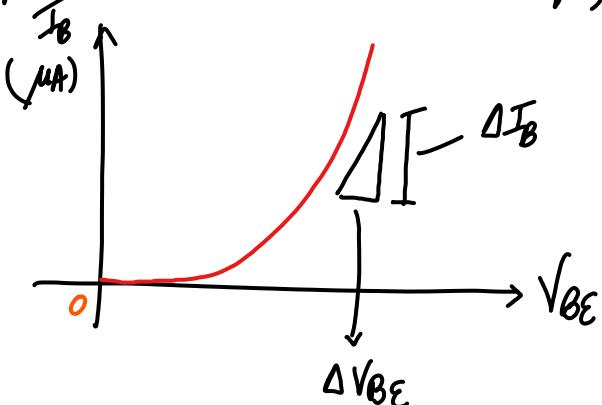

⑤ Output characteristics (V_{CE} Vs I_C at constant I_B value)

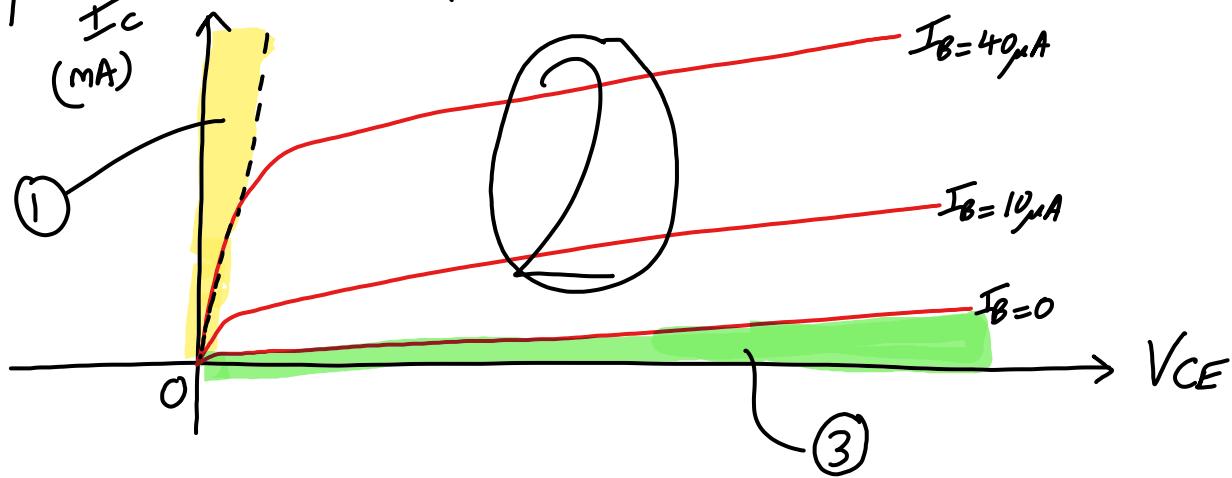

Region 1 - Saturation

Region 2 - Active

Region 3 - Cut-off

⑥ In active region \rightarrow As $I_B \uparrow_{\text{ses}} \rightarrow I_C \uparrow_{\text{ses}}$ ($I_C = \beta I_B$)

\rightarrow As $V_{CE} \uparrow_{\text{ses}} \rightarrow I_C$ also \uparrow_{ses} slightly

a) Since $V_{CE} = V_{CB} + V_{BE}$



b) V_{BE} being constant (I_B constant) \rightarrow As $V_{CE} \uparrow \rightarrow V_{CB} \uparrow_{\text{ses}}$



c) As $V_{CB} \uparrow_{\text{ses}}$, CB depletion layer width \uparrow_{ses}



d) \therefore Effective base width will reduce

(W_B')



e) i.e. I_B contribution will reduce (as less of electrons will recombine with holes in base region)




f) i.e. most of es travelling via base will be collected by collector

i.e. $I_C \uparrow_{\text{ses}}$

\therefore As $V_{CE} \uparrow_{\text{ses}} \rightarrow I_C \uparrow_{\text{ses}}$ with it

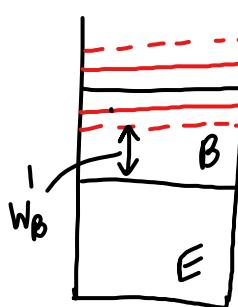(BJT is used as an amplifier in active region of bjt)



⑦ Since, I_B - I/p current , $I_C = \beta I_B$
 ↓
 I/p current

$\beta_{dc} = \frac{I_C}{I_B}$

" β_{dc} "
 CE current gain

β_{dc} almost same as β_{AC}

$\beta_{AC} = \frac{\Delta I_C}{\Delta I_B}$

⑧ In saturation region, as the value of V_{CE} reduces

a) $V_{CE} = V_{CB} + V_{BE}$

i.e As $V_{CE} \downarrow \rightarrow V_{CB} \downarrow$ sgn \downarrow constant

b) CB becomes lesser R.B & finally at very low value of $V_{CE} \rightarrow$ CB Jⁿ becomes F.B

c) BE Jⁿ is already F.B

d) As CB Jⁿ becomes F.B $\rightarrow e^-$ will not reach collector & $\therefore I_C$ reduces to zero as V_{CE} is reduced to lower value

e) i.e BJT operates in saturation region

g) npn bjt operates in cut-off region when $I_B = 0$
but here $I_C \neq 0$?

a) When $I_E = 0 \rightarrow$ leakage current $I_C = I_{CBO}$

$$\text{i.e } I_C = \alpha I_E + I_{CBO} - \textcircled{1}$$

$$\text{but } I_E = I_C + I_B$$

$$\text{i.e } I_C = \alpha (I_C + I_B) + I_{CBO}$$

$$(1-\alpha) I_C = \alpha I_B + I_{CBO}$$

$$\text{i.e } I_C = \frac{\alpha}{1-\alpha} I_B + \left(\frac{1}{1-\alpha}\right) I_{CBO}$$

$$\text{i.e } I_C = \beta I_B + \left(\frac{1}{1-\alpha}\right) I_{CBO}$$

In cut-off region $\rightarrow I_B = 0$

$$\therefore I_C \approx \left(\frac{1}{1-\alpha}\right) I_{CBO} \quad \frac{1}{1-\alpha} - \text{large value}$$

$$\text{i.e } I_C \approx (\beta + 1) I_{CBO} \quad \beta = \frac{\alpha}{1-\alpha}$$

$$1+\beta = \frac{1}{1-\alpha}$$

value of leakage
current at $I_B = 0$


Called as " I_{CEO} "

$$\text{i.e } I_{CEO} = (1+\beta) I_{CBO}$$

Collector to emitter
leakage current with base
open

⑩ Properties of CE configurations: .

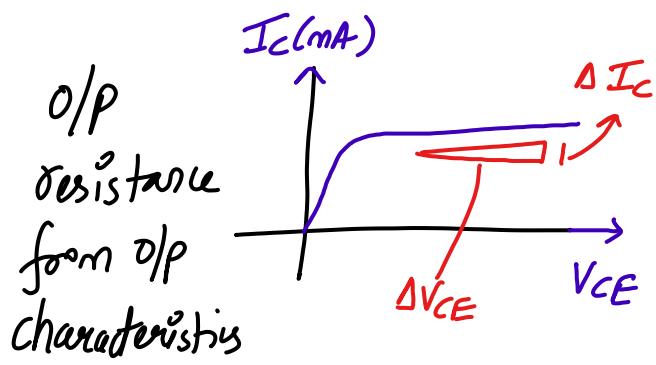- a) Moderate current gain
- b) Moderate voltage gain
- c) Moderate R_{in} & R_{out}
- d) High power gain



$$R_{out} = \frac{\Delta V_{CE}}{\Delta I_C} \quad | \quad I_B \text{ constant}$$

large value (in $k\Omega$)

_____ x _____

