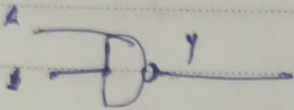



A	B	Y
0	0	1
1	0	0
0	1	0
1	1	0

$$Y = \bar{A} \cdot \bar{B} \quad \bar{A} \cdot \bar{B}$$



A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

$$Y = A \cdot B$$

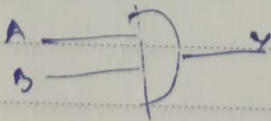

PREMIUM
CEMENT


BUILD WITH GOLD

Quad 2-Input NANDGATE


NOTES

DATE

20

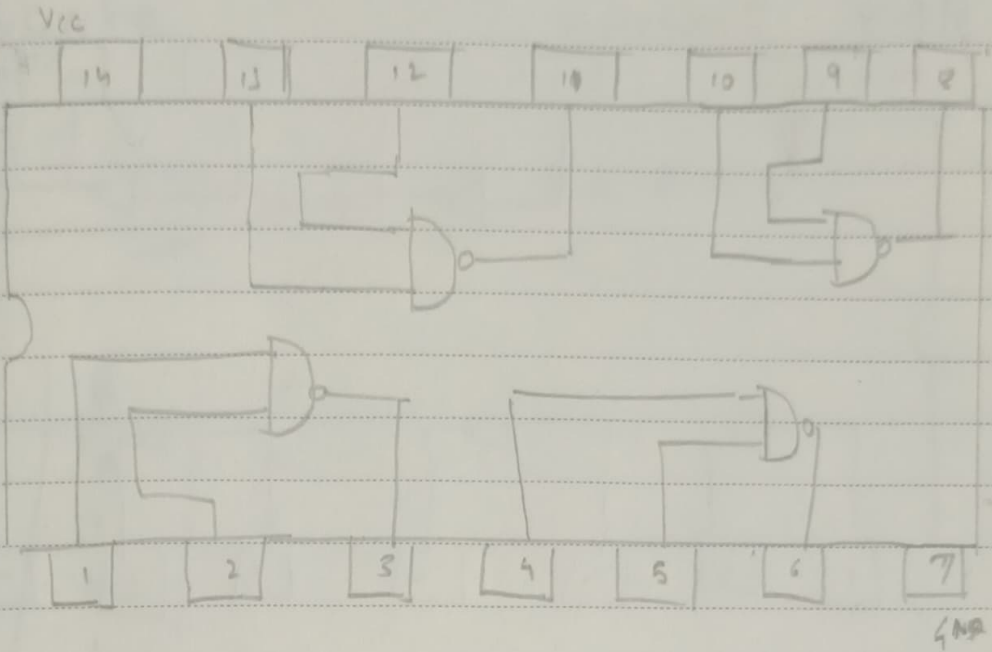


Quad 2-Input AND GATE

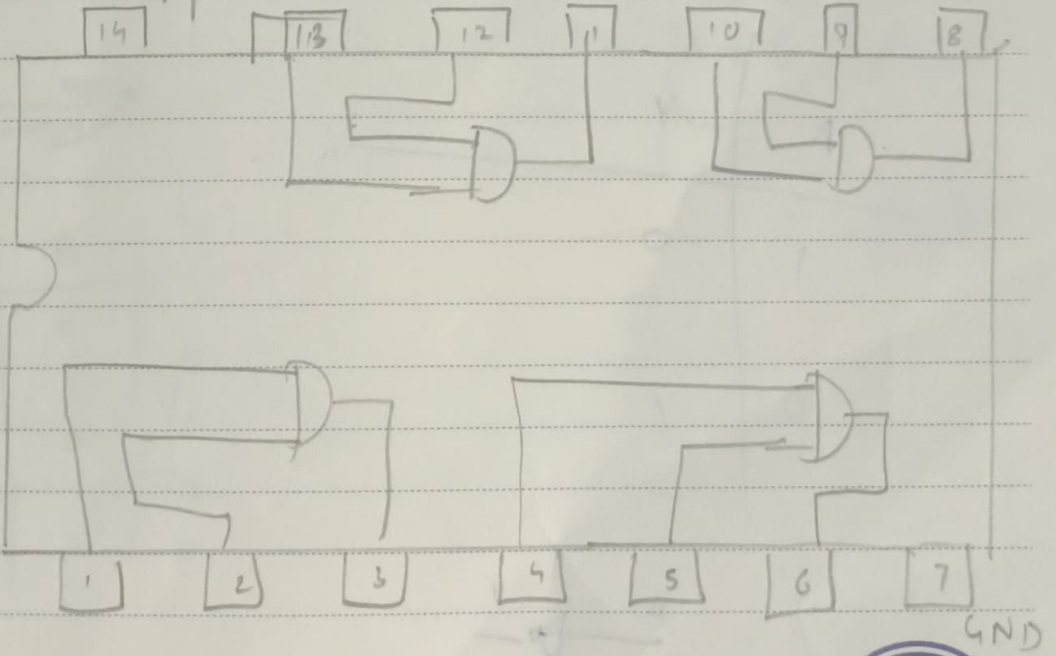

PREMIUM CEMENT


BUILD WITH GOLD

HE X Inverter

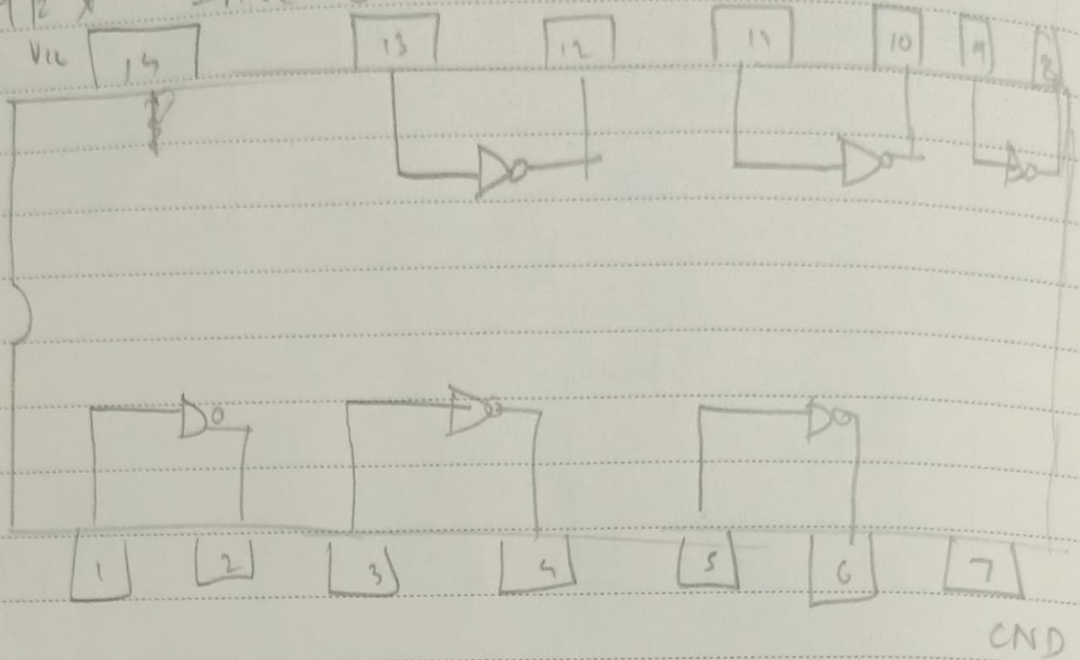

$$Y = \bar{A}$$

A	Y
1	0
0	1

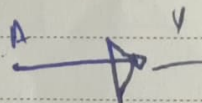

PREMIUM CEMENT

BUILD WITH GOLD


$$\bar{A}B + B\bar{A}$$

NOTES

DATE

20


OR Gate

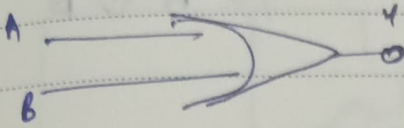

$$Y = A + B$$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

NOR gate

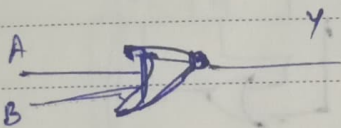

$$Y = \overline{A + B}$$

~~OR~~

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0




PREMIUM CEMENT


BUILD WITH GOLD

XOR

$$Y = A \oplus B$$


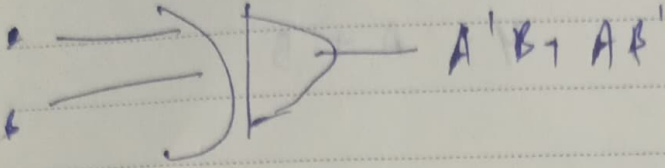


A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

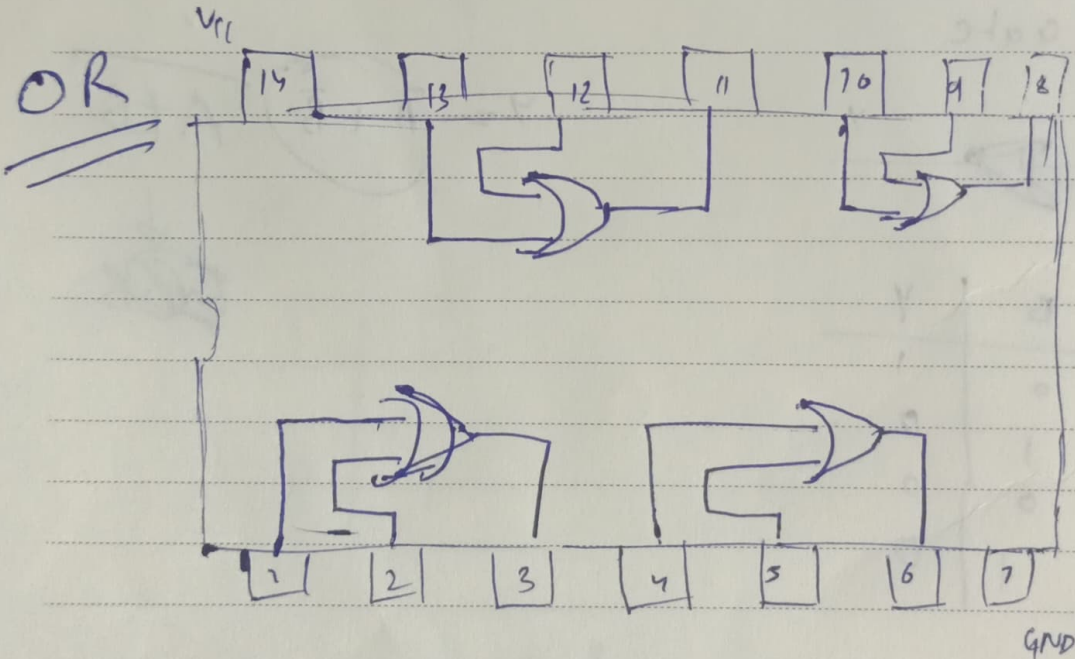

PREMIUM CEMENT

BUILD WITH GOLD

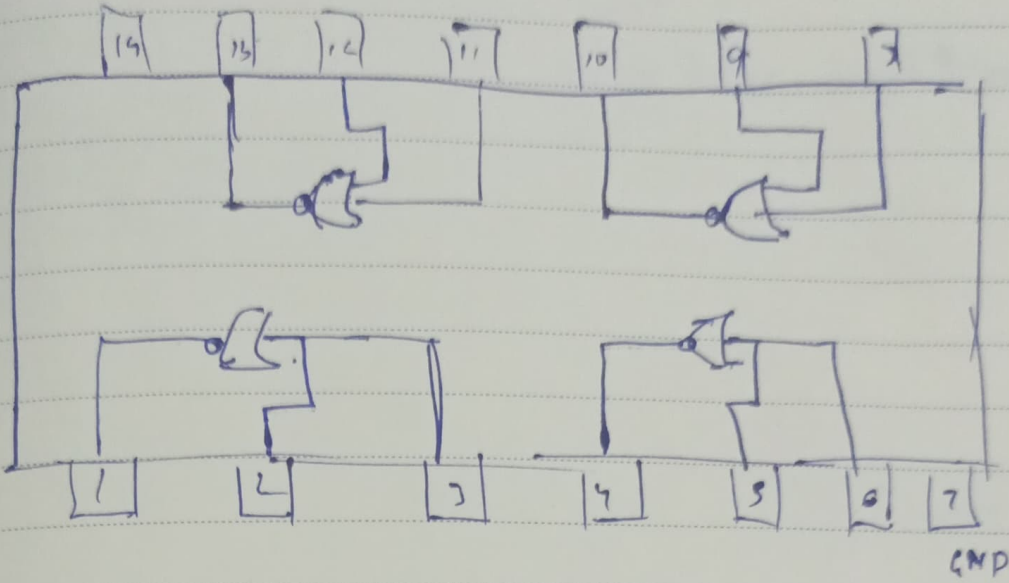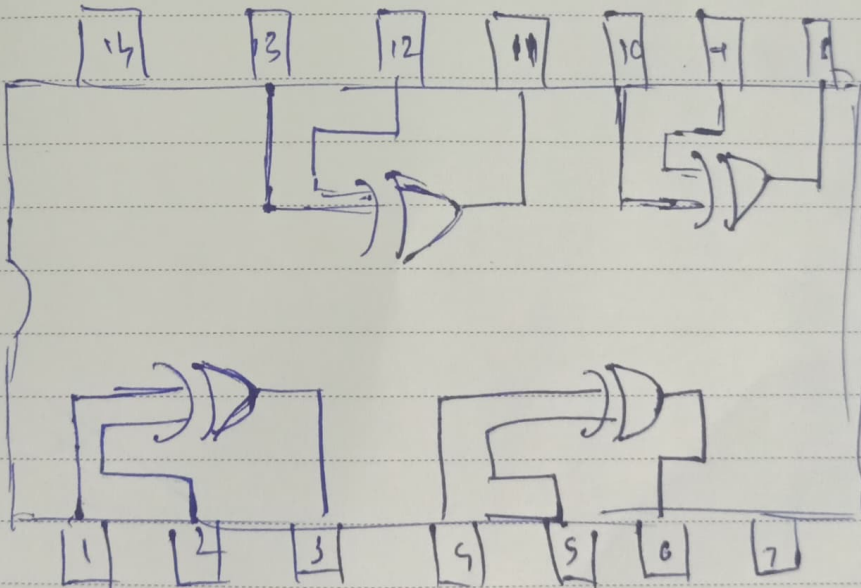NORNOR

PREMIUM
CEMENT


BUILD WITH GOLD

Basic Gates using Universal Gates


NAND : $Y =$

alan
21/8/21


→ AND ($Y = AB$)

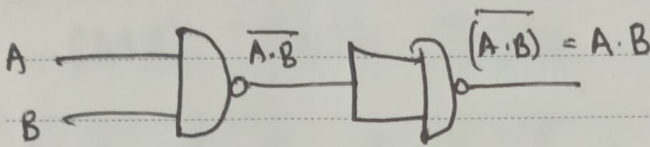


→ OR ($Y = A + B$)

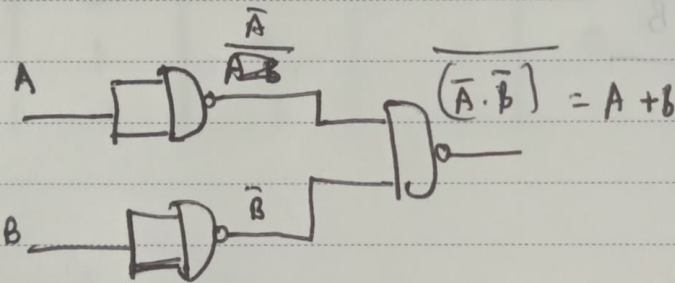




→ NOT ($Y = \bar{A}$)

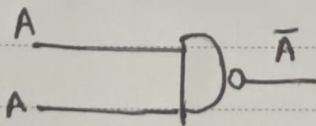


NOR ($Y = \overline{A + B}$)

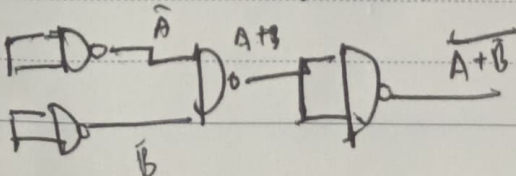

2] NOR

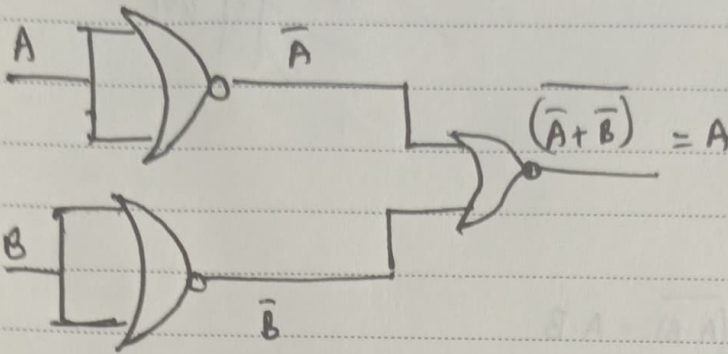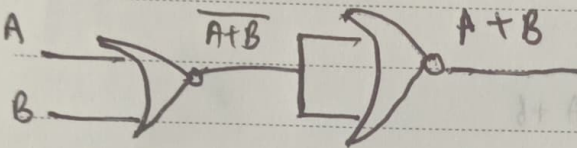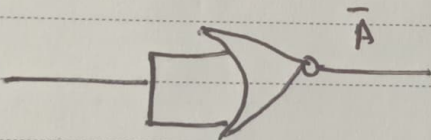→ AND ($Y = AB$)→ OR ($Y = A + B$)→ NOT ($Y = \bar{A}$)

→ NAND

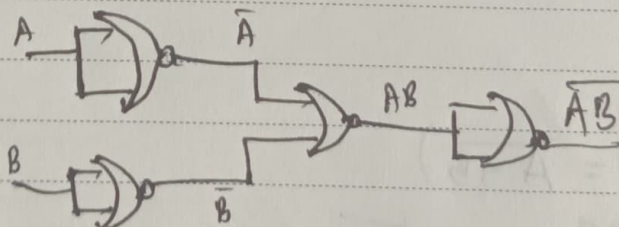

PREMIUM CEMENT

BUILD WITH GOLD