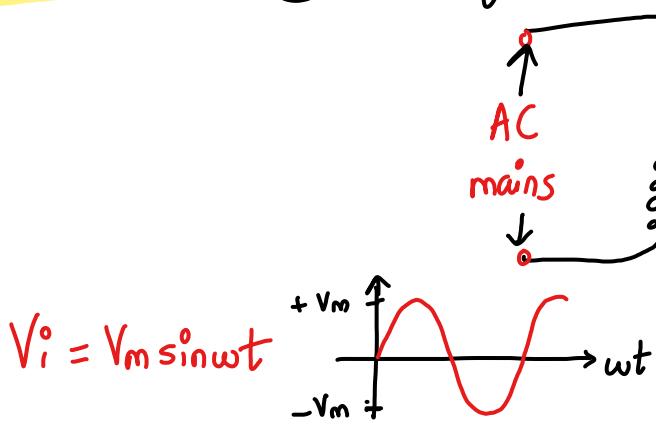


## # Full-wave bridge rectifier:




$V_i^o$ : Secondary transformer voltage  
"Two diodes conduct together"

$A^{+ve} - D_1 - R_L - D_3 - B$   
Iout path during +ve h.c



$D_1 \& D_3$ : ON (F.B)  
 $D_2, D_4$ : OFF (R.B)

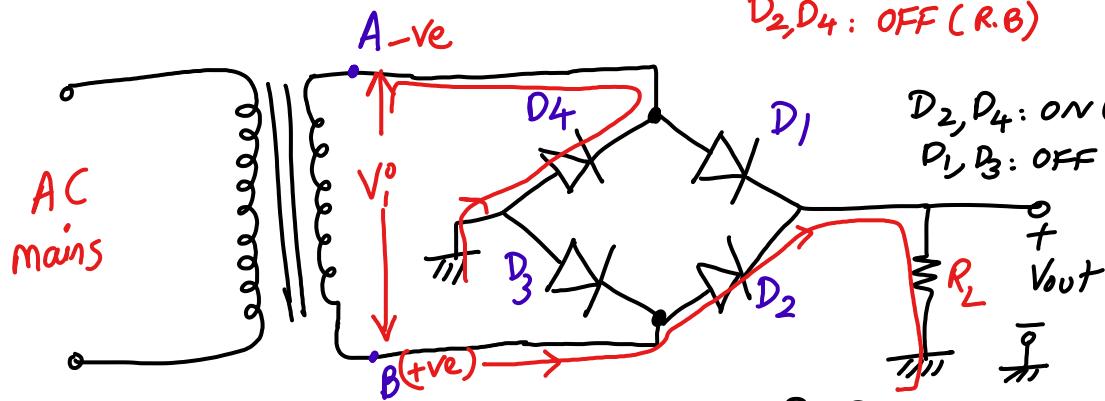$D_2, D_4$ : ON (F.B)  
 $D_1, D_3$ : OFF (R.B)




$$V_{out} = V_i^o (\text{if } 0 \leq wt \leq \pi) \\ = V_i^o (\text{if } \pi \leq wt \leq 2\pi)$$

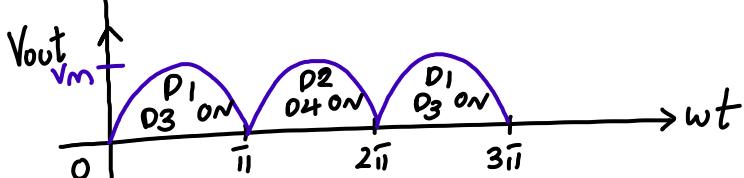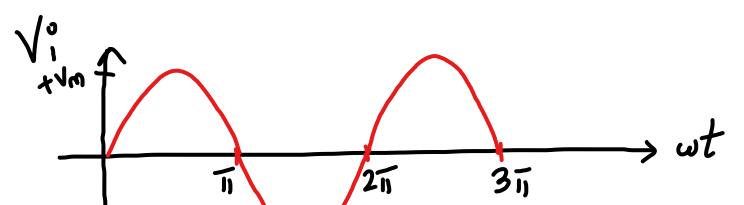$B - D_2 - R_L - D_4 - A$   
Iout path during -ve h.c



FWBR I/P-O/P  
waveform's

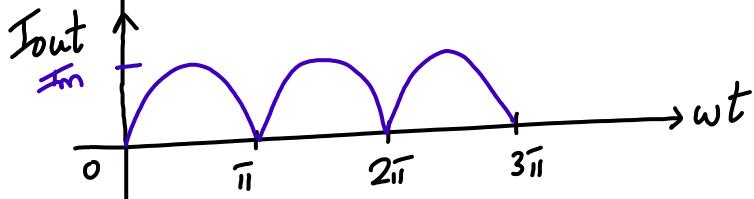

Due to 'R' load, nature of Vout & Iout are similar

## 'B' with 'R' load analysis:

Derive a) Expression for rectification efficiency ( $\eta$ )

b) Expression for ripple factor ( $\gamma$ )

c) Expression for TUF

$$\textcircled{1} \quad V_{\text{out(avg)}} = V_{\text{dc}} = \frac{1}{T} \int_0^T V_{\text{out}} \, dt$$

$$V_{\text{out(avg)}} = V_{\text{dc}} = \frac{2V_m}{\pi}$$

$$I_{\text{dc}} = \frac{2I_m}{\pi}$$

$$\textcircled{2} \quad I_{\text{out(avg)}} = \frac{V_{\text{out(avg)}}}{R_L} \quad (V_{\text{out(avg)}} = I_{\text{out(avg)}} R_L)$$

\textcircled{3} \quad V\_{\text{out(rms)}} \rightarrow \text{RMS value of AC component of output}

$$V_{\text{out(rms)}} = \left[ \frac{1}{T} \int_0^T V_{\text{out}}^2(wt) dwt \right]^{1/2}$$

$$\boxed{V_{\text{out(rms)}} = V_{\text{rms}} = \frac{V_m}{\sqrt{2}}} \quad \hookrightarrow \text{FWBR}$$

$$\boxed{I_{\text{rms}} = \frac{I_m}{\sqrt{2}}}$$

④ Rectification efficiency ( $\eta$ ):

$$\% \eta = \frac{P_{DC}}{P_{AC}} \times 100$$

It is the ratio of DC power at the output to the applied input AC power

$$P_{DC} = \frac{V_{dc}^2}{R_L}$$

$$\% \eta = \frac{\frac{4V_m^2}{\pi R_L}}{\frac{V_m^2}{2R_L}} \times 100$$

$$P_{AC} = \frac{V_{rms}^2}{R_L}$$

$$\boxed{\% \eta = \frac{8}{\pi^2} \times 100 = 81.05\%}$$

FWBR

## ⑤ Ripple factor ( $\gamma$ ):

It is the ratio of rms value of AC component to the DC component of the rectifier output

Smaller the AC component  $\rightarrow$  more effective is the rectifier

$$\gamma = \frac{I_{ac}}{I_{dc}}$$

$$; I_{ac} = \sqrt{I_{out(rms)}^2 - I_{dc}^2}$$

$$\text{i.e. } \frac{I_{ac}}{I_{dc}} = \sqrt{\frac{I_{rms}^2}{I_{dc}^2} - 1}$$

$$\text{i.e. } \boxed{\gamma = \sqrt{\frac{I_{rms}^2}{I_{dc}^2} - 1}}$$

for FWBR,

$$\gamma = \sqrt{\frac{\left(\frac{Im}{\sqrt{2}}\right)^2}{\left(\frac{2Im}{\pi}\right)^2} - 1}$$

$$\gamma = \sqrt{\frac{\frac{Im^2\pi^2}{4}}{2 \times 4 Im^2} - 1} = \sqrt{\frac{\pi^2}{8} - 1} = 0.483$$

$$\boxed{\gamma = 0.483 \text{ FWBR}}$$













