

EEEEE BJT CB configuration

12/11/23

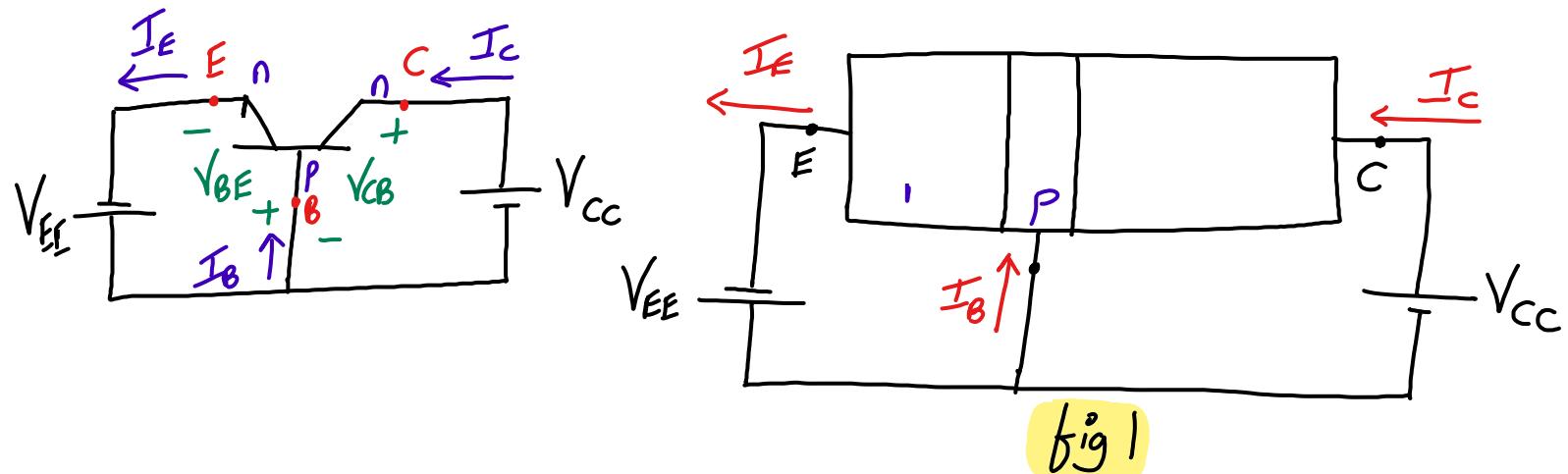


fig 1

- In common base (CB) configuration, input is applied between 'B' and 'E' and output is taken between 'C' and 'B'
- For BJT to be used as an amplifier \rightarrow npn bjt should be operated in active region

i.e B-E junction \rightarrow forward bias
and B-C junction \rightarrow reverse bias

- Terminal current in bjt,

$$I_E = I_C + I_B$$

- Behavior of bjt in CB mode can be described by two characteristics :
 - Input characteristics
 - Output characteristics

⑤ I_E : input current

V_{BE} : input voltage

Input characteristics:

V_{BE} Vs I_E at fixed V_{CB}


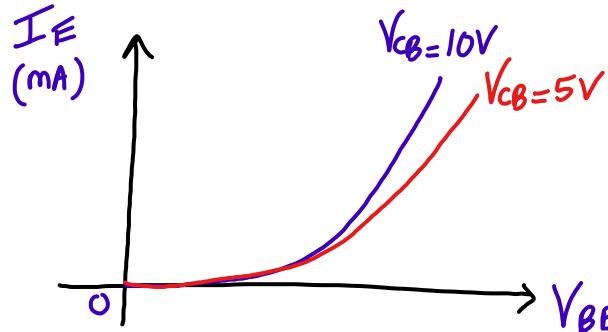


fig2: I/P characteristics
in npn bjt in CB mode

⑥ Fig 2 shows input characteristics of npn bjt in CB mode → it is similar to forward characteristics in PN junction diode

(Since BE junction is made of PN junction) (fig 1)

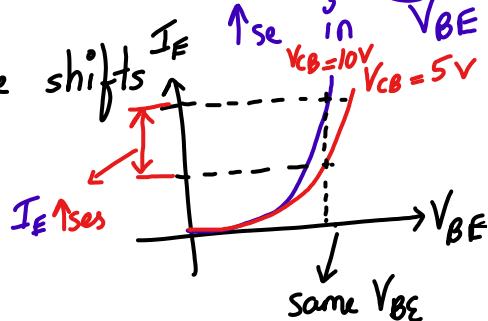⑦ As $V_{BE} \uparrow$ ses → it will F.B. B.E junction more → more carriers es will reach collector (as V_{CB} is fixed)
and $I_E \uparrow$ ses exponentially with (CB Jⁿ is reverse-biased)



Reason:

a) As CB junction gets more R.B

b) Width of CB depletion region will ↑se


c) So, less voltage is required to F.B BE junction

Thus, curve shifts to L.H.S ie for same V_{BE} → $V_{CB} \uparrow$ ses from 5V to 10V current $I_E \uparrow$ ses slightly


⑨ From input characteristics, we can find the input impedance of the device

$$R_{in}^o = \frac{\Delta V_{BE}}{\Delta I_E}$$

small chan
V_{CB} constant
huge changes

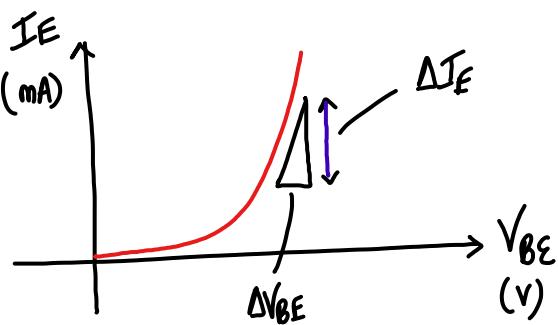

Thus, R_{in}^o is very low (in ohms) for npn BJT in CB configuration

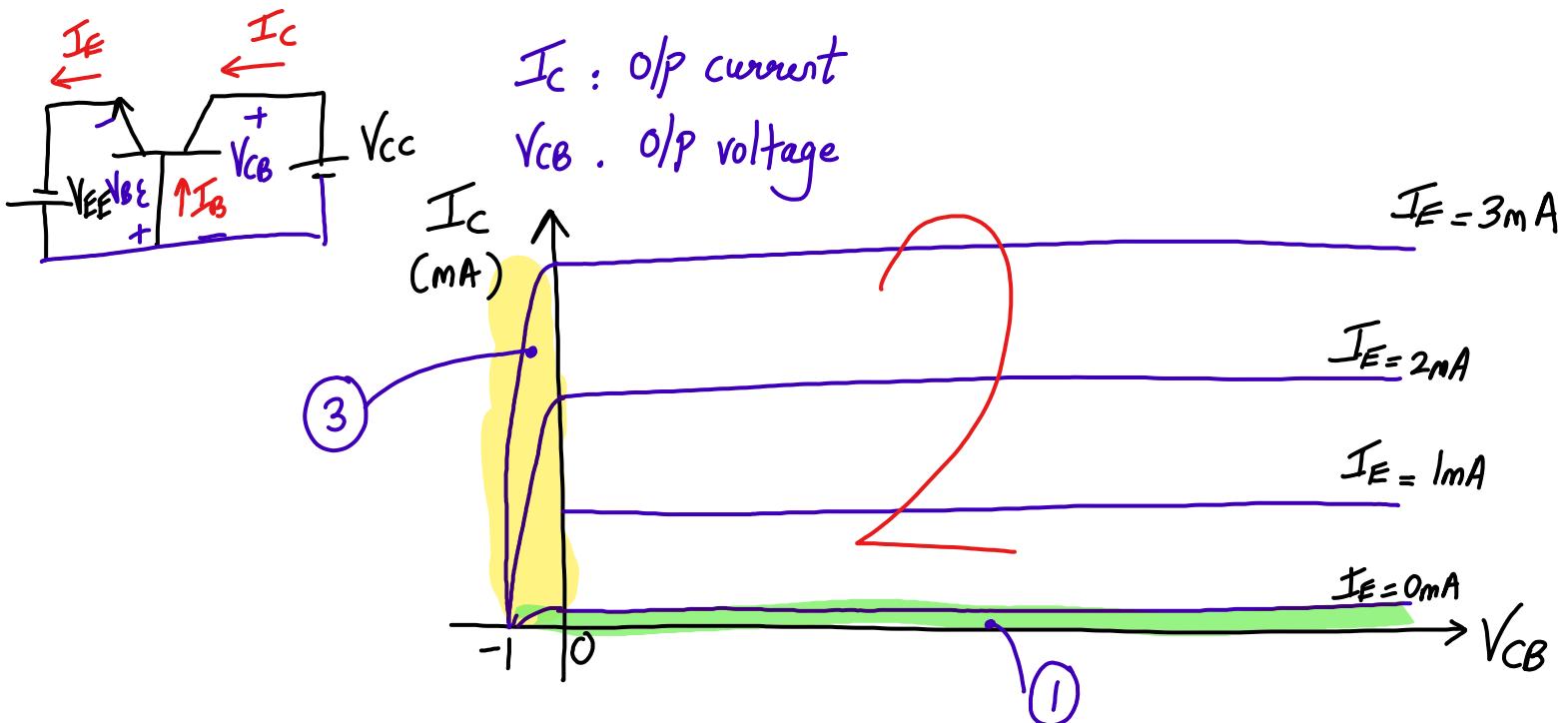


Region 1 : Cut-off

Region 2 : Active

Region 3 : Saturation

fig 3 : Output characteristics of npn bjt
in CB configuration

V_{CB} Vs I_c | I_E constant

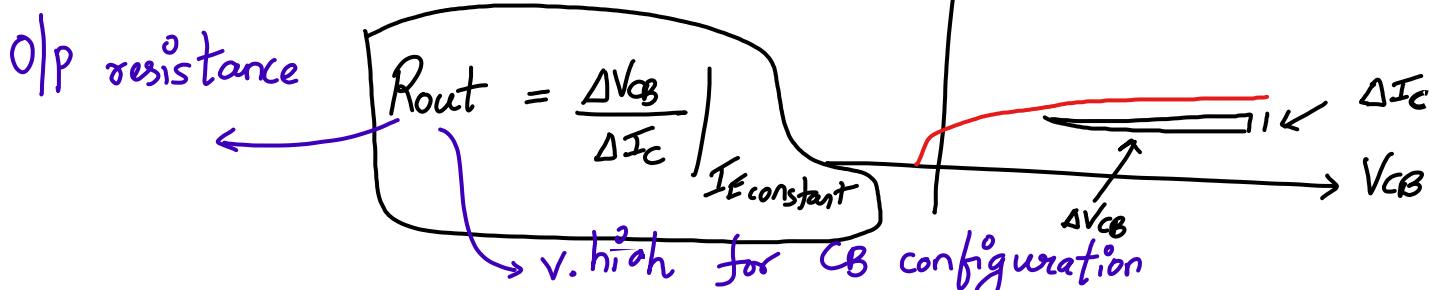

a) In active region $\rightarrow I_C$ is constant due to constant V_{BE}

Even if $V_{CB} \uparrow$ $\rightarrow I_C = \alpha I_E$ remains almost constant

$CB J^n$ becomes more R.B

$I_C = \alpha I_E$
o/p current
I/P current

npn bjt behaves like a constant current source

(Due to this, this region is used amplification purposes.)

b) In cut-off region $\rightarrow I_E = 0mA$ \rightarrow As $V_{CB} \uparrow$, I_C remain almost at 0mA

\downarrow as $V_{EE} = 0V \rightarrow I_E = 0, I_C \approx 0$

But I_C will exist due to minority charge carriers (as $CB J^n$ is R.B) only (I_{CBO})

$$I_C = \alpha I_E + I_{CBO}$$

i.e. $I_C \approx I_{CBO}$

I_{CBO} leakage current


reverse saturation current with emitter open

c) In saturation region \rightarrow as we reduce value of V_{CB} (i.e less R.B)

I_C starts reducing

(Since as R.B is $\downarrow \rightarrow e^-$ which have entered into B from E will removed betⁿ C & B will not be able to cross collector $\rightarrow \therefore I_C$ reduces)
i.e here $BC J^n$ & $BC J^n \rightarrow$ both are F.B \rightarrow saturation region

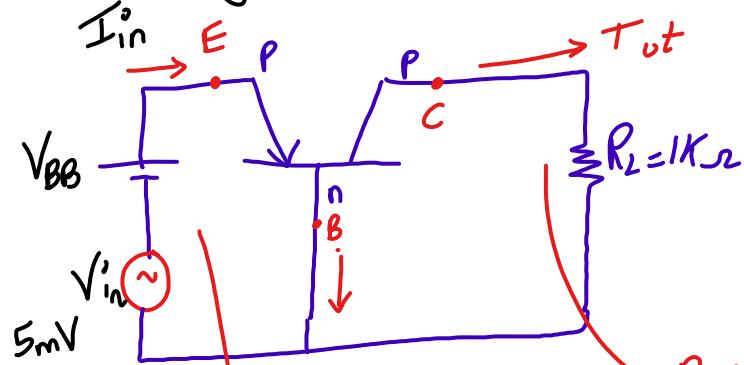10) How signal is getting amplified in CB configuration



R_{in}^o low (say 10Ω)

$$I_{in}^o = \frac{mV}{10} = 0.5mA$$

$$\alpha = 1 \quad (I_C = \alpha I_E)$$

$$I_C \approx I_E$$

$$I_{out} = I_{in}^o = 0.5mA$$

$$V_{out} = I_{out} R_L$$

$$= 0.5mA \times 1k\Omega$$

$$V_{out} = 0.5V - 500mV$$

$$A_v = \frac{V_{out}}{V_{in}} = \frac{50mV}{5mV} = 100$$

i.e Input signal got amplified by factor of 100 (Typ: 50-300)

→ Current gain $I_C = I_E$

$$\alpha \approx \frac{I_C}{I_E} \approx 1$$

— X —

